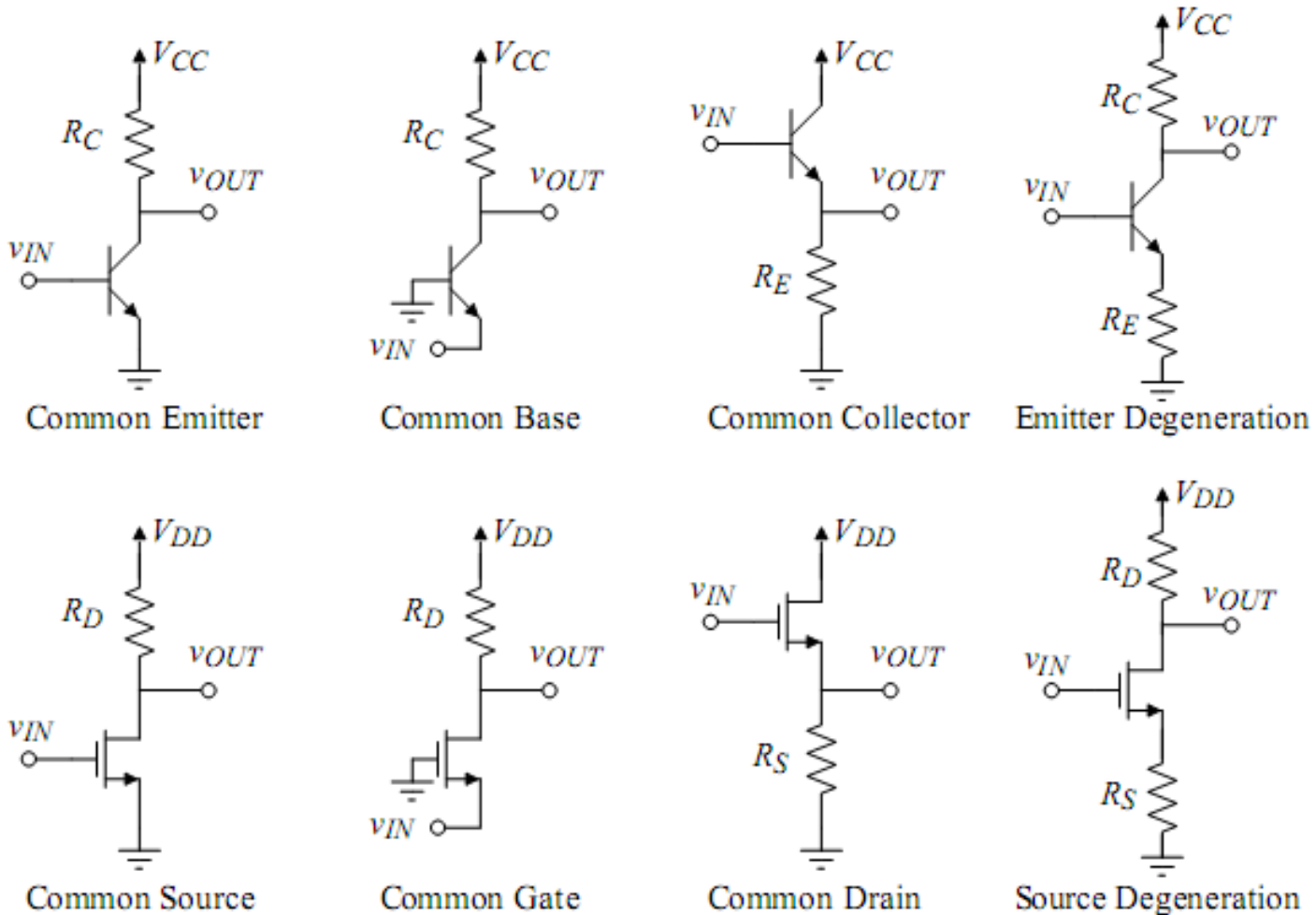





# Review of CMOS amplifiers

Apinunt Thanachayanont

# Basic CMOS amplifiers




# Common-source amplifier

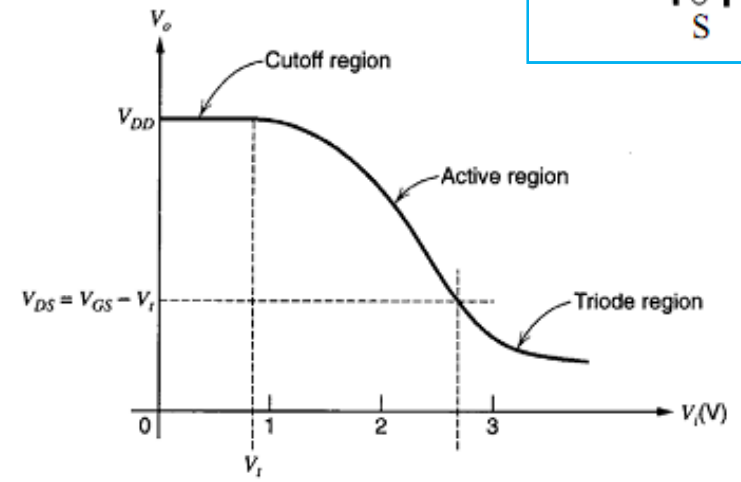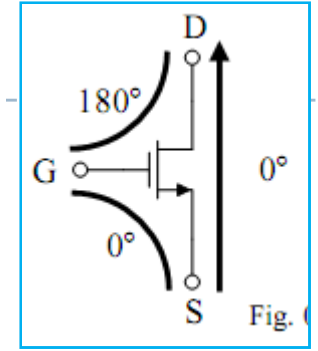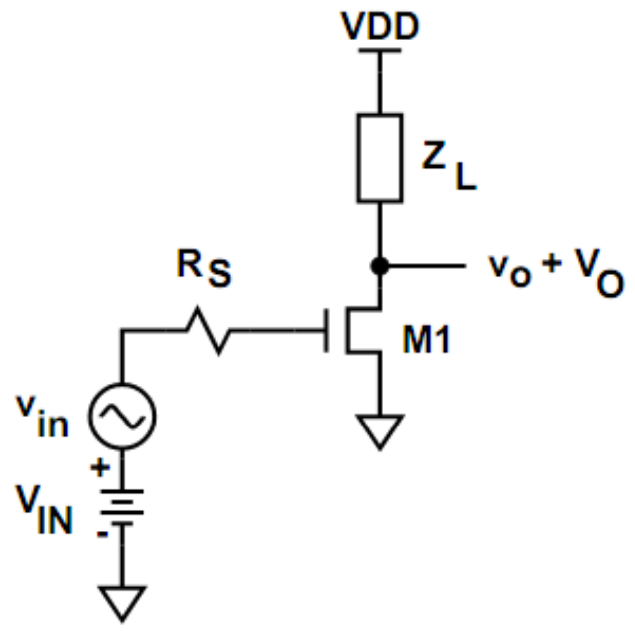

$$V_o = V_{DD} - I_d \cdot R_L = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_i - V_{tn})^2 \cdot R_L$$

- DC voltage  $V_i$  is chosen to bias M1 so that M1 is in active (saturation) region and its drain voltage is near the midpoint of the output swing ( $V_o \approx V_{DD}/2$ ).
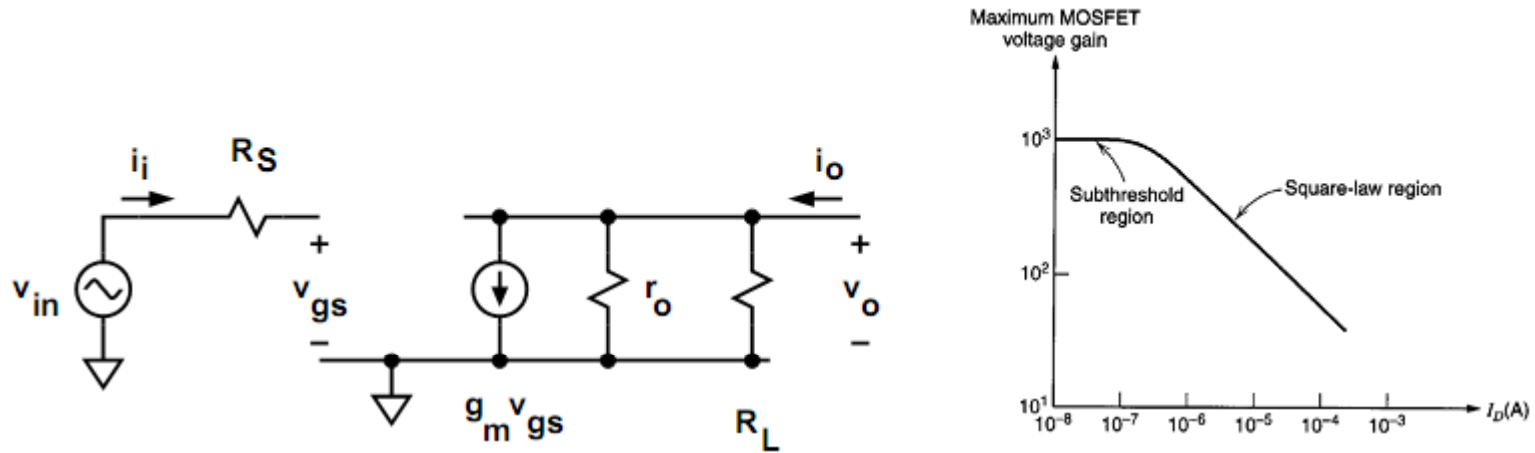
# Common-source amplifier – small-signal analysis




$$A_v(0) = -g_m(r_o \parallel R_L) = -g_m R'_L \quad R_i = \infty \quad R_o = r_o \parallel R_L = R'_L$$

- Note that for  $R_L \rightarrow \infty$ ,  $R'_L \rightarrow r_o$ , and


$$|A_v(0)|_{max} = g_m r_o = \frac{I_D}{V_{ov}/2} \times \frac{L_{eff}}{I_D} \left| \frac{\partial L_{eff}}{\partial V_{DS}} \right|^{-1} = \frac{2L_{eff}}{V_{ov}} \left| \frac{\partial L_{eff}}{\partial V_{DS}} \right|^{-1}$$
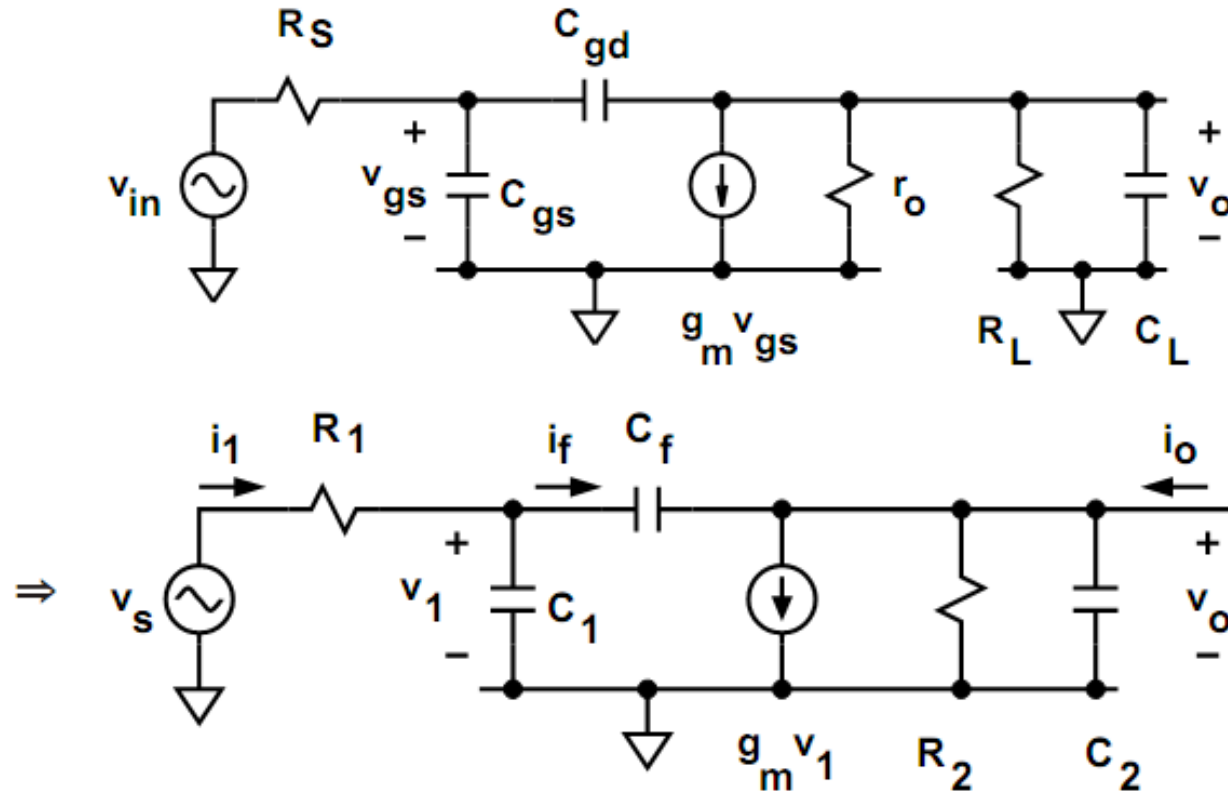
# Common-source amplifier – small-signal analysis



$$v_s = v_i \quad R_1 = R_S \quad R_2 = r_o \parallel R_L \quad C_1 = C_{gs} \quad C_2 = C_L \quad C_f = C_{gd}$$

# Miller approximation

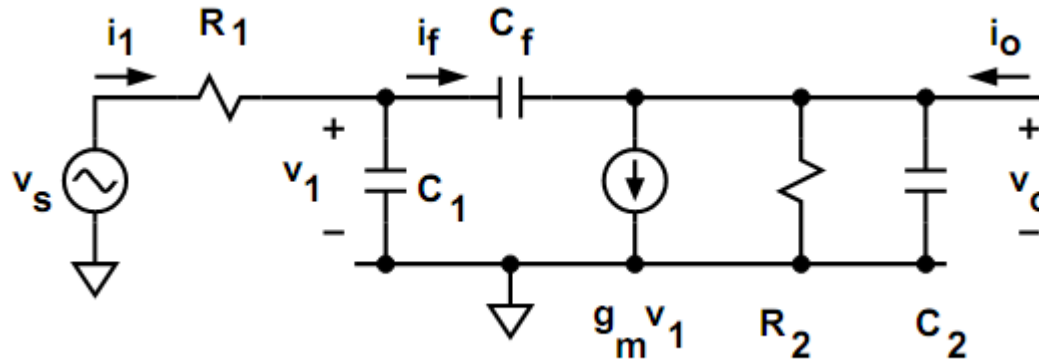


$$v_o = (-g_m v_1 + i_f) \left( R_2 \parallel \frac{1}{sC_2} \right) \quad i_f = (v_1 - v_o) s C_f$$

If  $R_2$ - $C_2$  is a non-dominant pole, then, at the frequencies of interest

$$v_o \approx -g_m R_2 v_1 \quad i_f \approx (v_1 + g_m R_2 v_1) s C_f \quad \Rightarrow \quad \frac{i_f}{v_i} = s(1 + g_m R_2) C_f = s C_M$$

$$C_M = (1 + g_m R_2) \cdot C_f = (1 + a_{v0}) \cdot C_f = \text{Miller Capacitance}$$

# Miller approximation

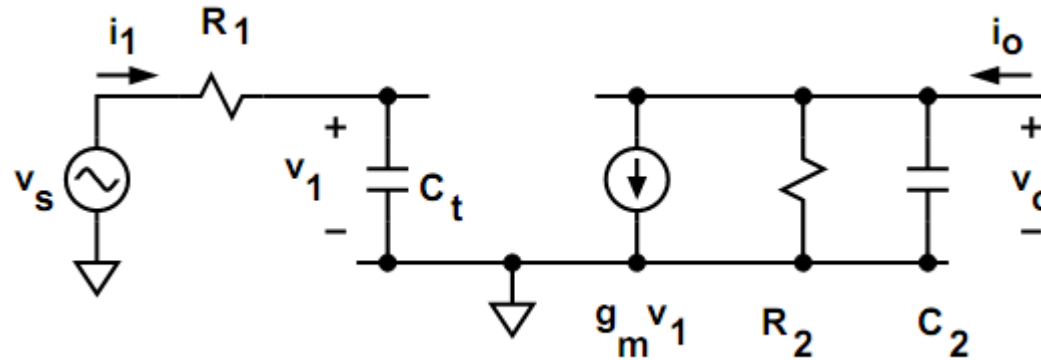


$$C_t = C_1 + C_M = C_1 + (1 + g_m R_2) C_f$$

$$A_v(s) = \frac{V_o}{V_s} = A_v(0) \frac{1}{(1 - s/p_1)(1 - s/p_2)}$$

$$A_v(0) = -g_m R_2 \quad p_1 = \frac{1}{R_1 C_t} \quad p_2 = \frac{1}{R_2 C_2}$$

# MOSFET's Transition frequency

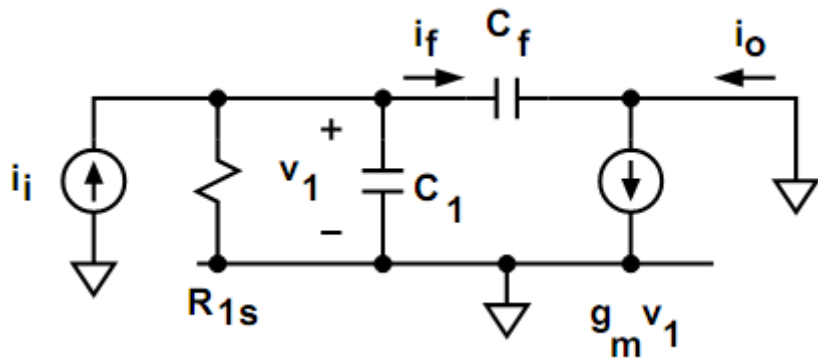

$$i_o \approx -g_m \times v_1 = -g_m \times i_i \frac{R_{1s}}{1 + R_{1s}(C_1 + C_f)s}$$

$$\text{Short-Circuit Current Gain} = \beta(s) = -\frac{i_o}{i_i} = \frac{g_m R_{1s}}{1 + R_{1s}(C_1 + C_f)s}$$

$$\text{Transition Frequency} = \omega_T \approx \frac{g_m}{C_1 + C_f}$$

$$R_{1s} = \infty \quad C_1 = C_{gs} = \frac{2}{3}C_{ox}WL \quad C_f = C_{gd}$$

$$\omega_T = 2\pi f_T = \frac{g_m}{C_{gs} + C_{gd}}$$

# MOSFET's Transition frequency

---

To calculate intrinsic device speed, let  $\omega_T \approx g_m/C_{gs}$ .

- For square-law device,

$$g_m = \mu C_{ox} \frac{W}{L} V_{ov} \quad \Rightarrow \quad \omega_T = \frac{3}{2} \cdot \frac{\mu}{L^2} \cdot V_{ov}$$

- For device with carrier velocity saturation,

$$g_m = W C_{ox} v_{scl} \quad \Rightarrow \quad \omega_T = \frac{3}{2} \cdot \frac{v_{scl}}{L}$$

# MOSFET's Transition frequency

---

For MOSTs in the weak inversion region,

$$\omega_T = \frac{g_m}{C_{gb}} \quad g_m = \frac{I_D}{U_T} \frac{C_{ox}}{C_{ox} + C_{depl}} \quad C_{gb} = WL \times \frac{C_{ox}C_{depl}}{C_{ox} + C_{depl}}$$


$$\omega_T = \frac{I_D}{U_T} \cdot \frac{1}{WLC_{depl}} = \frac{I_t}{U_T} \cdot \frac{1}{C_{depl}} \cdot \frac{1}{L^2} \cdot \frac{I_D}{I_M}$$

- $I_M = I_t \cdot W/L$  is the maximum  $I_D$  for device in weak inversion.

Since  $I_t \propto D_n$  and  $D_n = \mu U_T$ , we have

$$\omega_T \simeq \frac{D_n}{L^2} \cdot \frac{I_D}{I_M} \simeq \frac{\mu}{L^2} \cdot U_T \cdot \frac{I_D}{I_M}$$
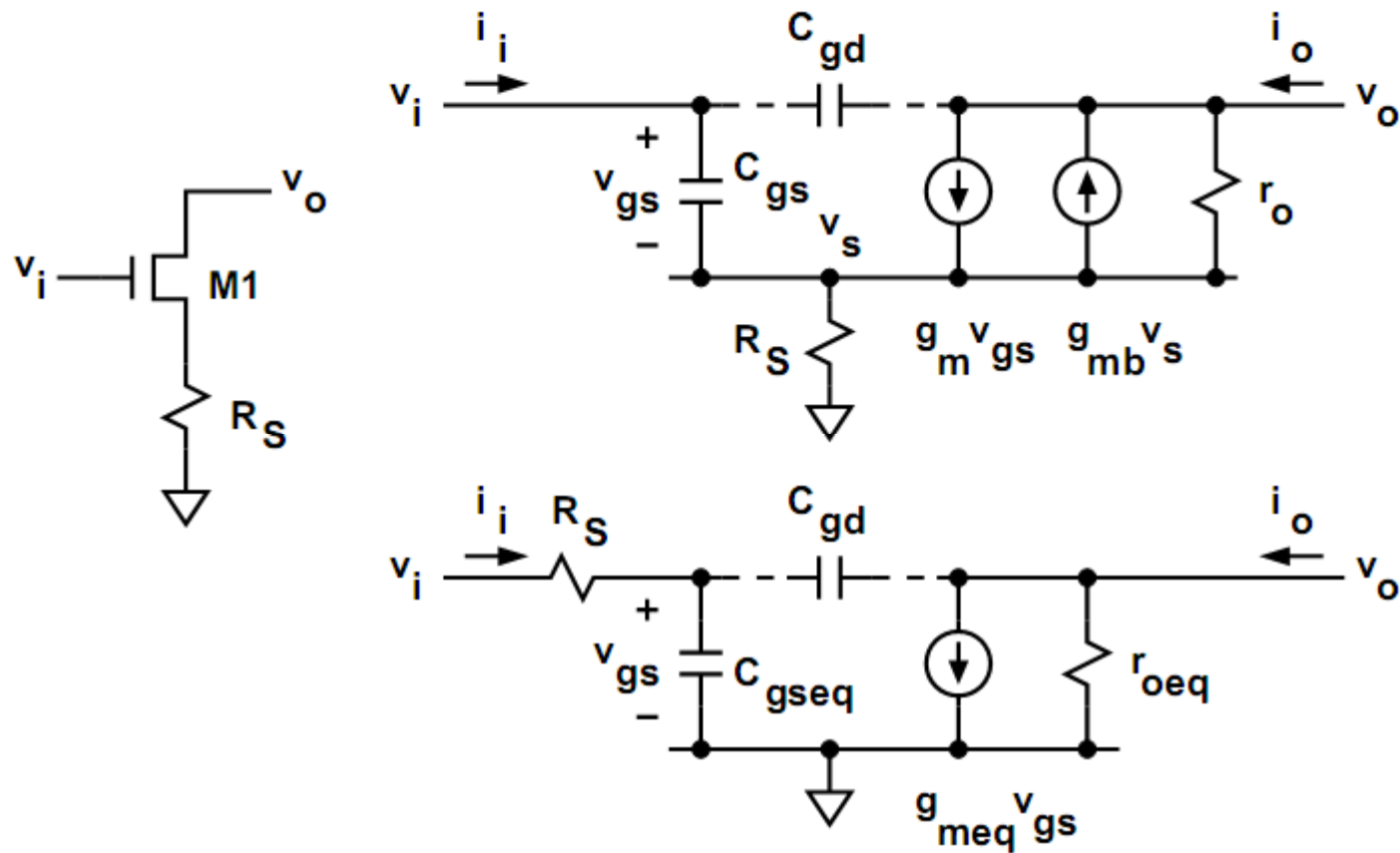
# Common-source amplifier with source degeneration



# Common-source amplifier with source degeneration

---

To find  $C_{g_{seq}}$  and  $g_{meq}$ , let  $v_o = 0$ , then

$$(g_m + sC_{gs})(v_i - v_s) = (G_S + g_{mb} + g_o)v_s$$

At frequencies where  $\omega \ll \omega_T = g_m/C_{gs}$ ,

$$\frac{v_s}{v_i} = \frac{g_m + sC_{gs}}{g_m + g_{mb} + G_S + g_o + sC_{gs}} \approx \frac{g_m}{g_m + g_{mb} + G_S + g_o}$$

$$g_{meq} = \frac{-i_o}{v_i} = g_m \left(1 - \frac{v_s}{v_i}\right) - (g_{mb} + g_o) \frac{v_s}{v_i} = \frac{g_m G_S}{g_m + g_{mb} + G_S + g_o} = \frac{g_m}{1 + (g_m + g_{mb})R_S + \frac{R_S}{r_o}}$$

$$\frac{i_j}{v_i} = sC_{gs} \left(1 - \frac{v_s}{v_i}\right) = sC_{gs} \cdot \frac{1 + g_{mb}R_S + \frac{R_S}{r_o}}{1 + (g_m + g_{mb})R_S + \frac{R_S}{r_o}}$$

# Common-source amplifier with source degeneration

---

- If  $r_o \gg R_S$ ,

$$g_{meq} \approx \frac{g_m}{1 + (g_m + g_{mb})R_S} = \frac{g_m}{1 + (1 + \chi)g_m R_S}$$

$$C_{gseq} = C_{gs} \cdot \frac{1 + g_{mb}R_S}{1 + (g_m + g_{mb})R_S} = C_{gs} \cdot \frac{1 + \chi g_m R_S}{1 + (1 + \chi)g_m R_S}$$

To find  $r_{oeq}$ , let  $v_i = 0$ , then

$$(g_m + g_{mb} + sC_{gs} + G_S)v_s = g_o(v_o - v_s)$$


$$\frac{v_s}{v_o} = \frac{g_o}{g_m + g_{mb} + G_S + g_o + sC_{gs}} \approx \frac{g_o}{g_m + g_{mb} + G_S + g_o}$$

$$g_{oeq} = \frac{i_o}{v_o} = g_o \left( 1 - \frac{v_e}{v_o} \right) - (g_m + g_{mb}) \frac{v_e}{v_o} = \frac{g_o G_S}{g_m + g_{mb} + G_S + g_o}$$

$$r_{oeq} = R_S + r_o [1 + (g_m + g_{mb})R_S]$$

- $r_{oeq}$  can be made arbitrarily large by increasing  $R_S$ .

# Common-gate amplifier

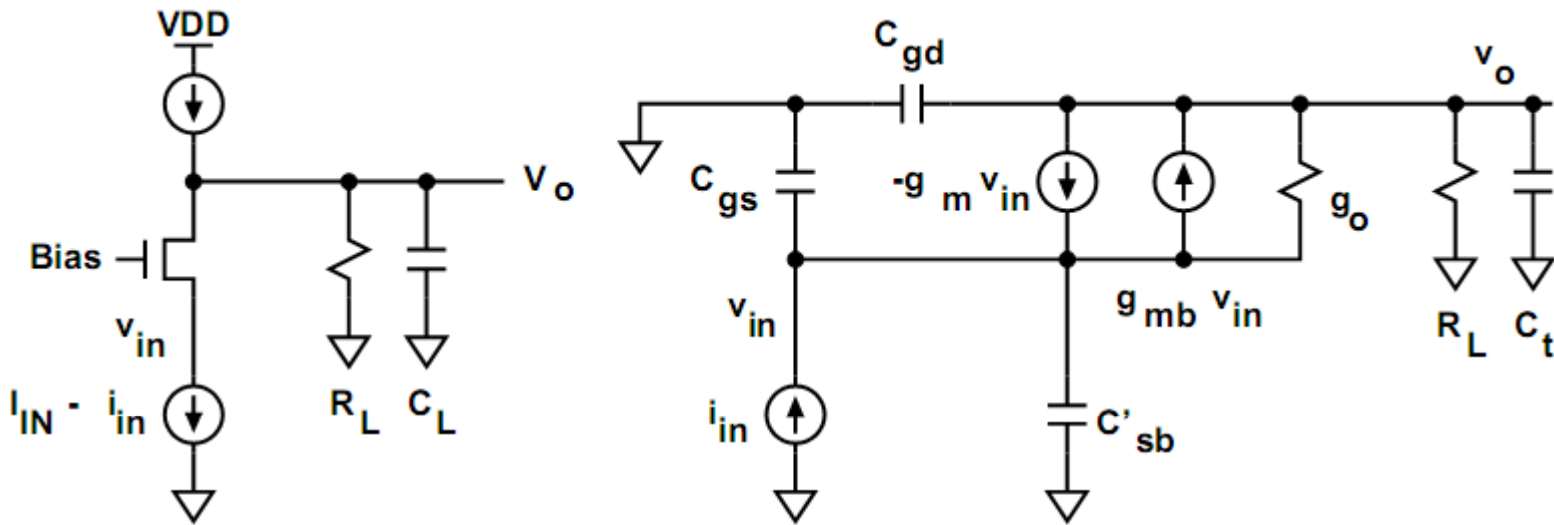

$$g'_m = g_m + g_{mb} \quad C'_L = C_t + C_{gd} = C_L + C_{db} + C_{gd} \quad C_{in} = C_{gs} + C'_{sb}$$

The nodal equations are

$$i_{in} = (g'_m + sC_{in})v_{in} - g_o(v_o - v_{in}) \quad g'_m v_{in} = (G_L + sC'_L)v_o + g_o(v_o - v_{in})$$

# Common-gate amplifier

---

If the  $g_o(v_o - v_{in})$  terms are neglected, then

$$\text{Transimpedance} = Z_t(s) = \frac{v_o}{i_{in}} = \frac{R_L}{(1 - s/p_1)(1 - s/p_2)}$$

$$p_1 = -\frac{g'_m}{C_{in}} = -\frac{g'_m}{C_{gs} + C'_{sb}} \quad p_2 = -\frac{1}{R_L C'_L}$$

$$\text{Input Impedance} = Z_{in}(s) = \frac{v_{in}(s)}{i_{in}(s)} = \frac{1/g'_m}{1 - s/p_1}$$

$$\text{Current Gain} = \frac{i_o(s)}{i_{in}(s)} = \frac{g'_m v_{in}}{i_{in}} = g'_m Z_{in}(s) = \frac{1}{1 - s/p_1}$$

- Note that  $p_1 \simeq \omega_T = g_m / (C_{gs} + C_{gd})$ .

# Common-gate amplifier

---

If  $g_o$  is considered,

$$\text{Voltage Gain} = A_v(s) = \frac{v_o}{v_{in}} = \frac{g'_m + g_o}{g_o + G_L + sC'_L}$$

$$\text{Input Impedance} = Y_{in}(s) = \frac{i_{in}}{v_{in}} = g'_m + sC_{in} - g_o(A_v - 1)$$


$$Z_t(s) = \frac{v_o}{i_{in}} = \frac{A_v(s)}{Y_{in}(s)}$$

- At low frequencies where  $\omega \rightarrow 0$ , assuming  $g'_m \gg g_o$ ,

$$A_v = \frac{g'_m + g_o}{g_o + G_L} \approx \frac{g'_m}{g_o + G_L}$$

$$\Rightarrow Y_{in} = g'_m - \frac{g'_m}{1 + \frac{G_L}{g_o}} + g_o \approx \frac{g'_m}{1 + \frac{R_L}{r_o}} \quad Z_t = \frac{A_v}{Y_{in}} \approx R_L$$

# Common-drain amplifier

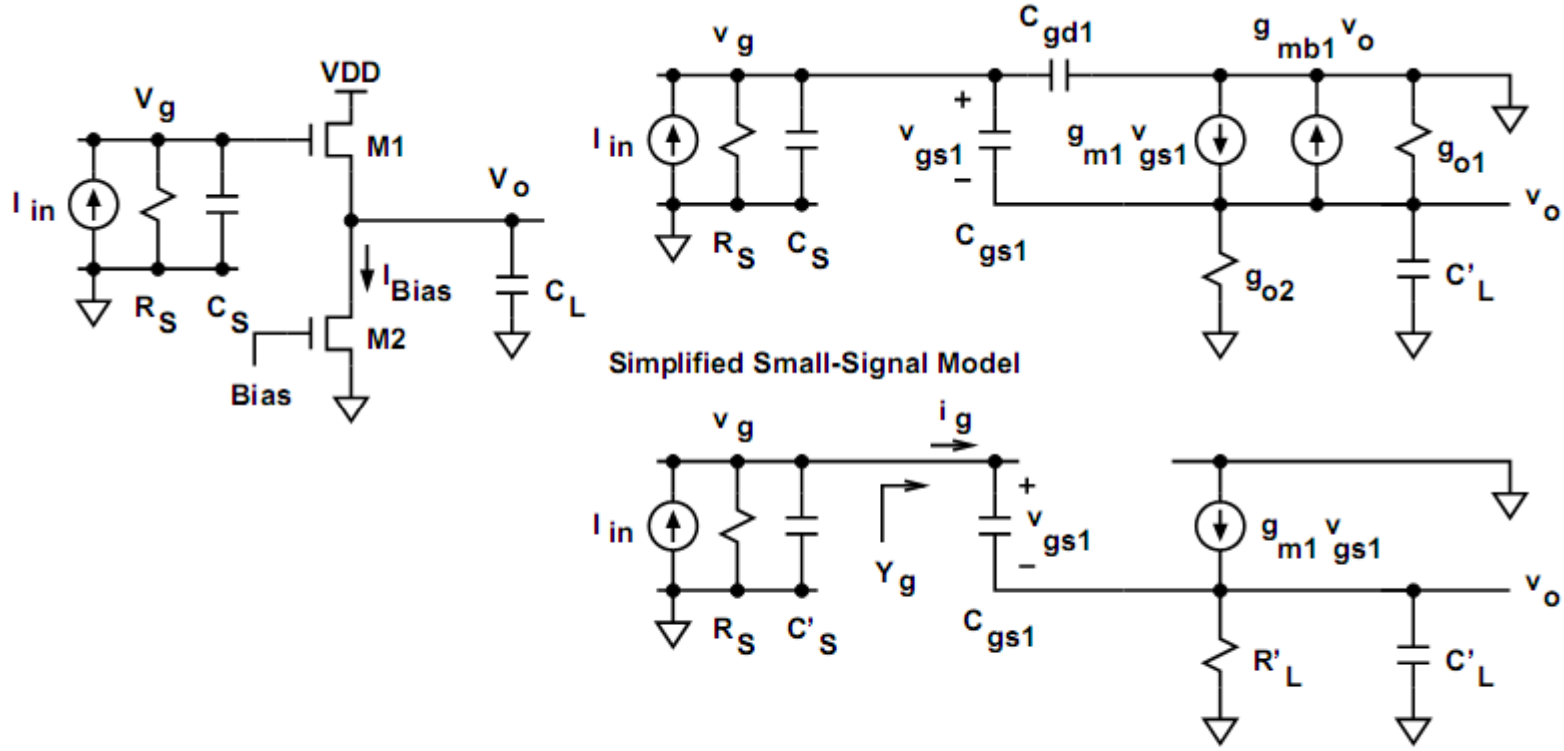

$$C'_S = C_S + C_{gd1} \quad C'_L = C_L + C'_{sb1} + C_{db2} + C_{gd2} \quad G'_L = g_{o1} + g_{o2} + g_{mb1} = \frac{1}{R'_L}$$

# Common-drain amplifier

---

Summing the currents at the output node, we have

$$(g_{m1} + sC_{gs1})(v_g - v_o) - v_o(sC'_L + G'_L) = 0$$

The voltage gain from gate to output is

$$A_{vg}(s) \equiv \frac{v_o(s)}{v_g(s)} = \frac{g_{m1} + sC_{gs1}}{g_{m1} + G'_L + s(C_{gs1} + C'_L)} = A_{vg}(0) \frac{1 - s/z_1}{1 - s/p_1}$$

$$A_{vg}(0) = \frac{g_{m1}}{g_{m1} + G'_L} = \frac{g_{m1}}{g_{m1} + g_{mb1} + g_{o1} + g_{o2}} \quad A_{vg}(\infty) = \frac{C_{gs1}}{C_{gs1} + C'_L}$$
$$z_1 = -\frac{g_{m1}}{C_{gs1}} \approx -\omega_T \quad p_1 = -\frac{g_{m1} + G'_L}{C_{gs1} + C'_L}$$

# Common-drain amplifier

For most practical cases

$$g_{o1} + g_{o2} \ll g_{m1} + g_{mb1} = g_{m1}(1 + \chi)$$


$$A_{vg}(0) \approx \frac{g_{m1}}{g_{m1} + g_{mb1}}$$

$$\approx \frac{1}{1 + \chi_1}$$


$$p_1 \approx -\frac{g_{m1}(1 + \chi_1)}{C_{gs1} + C'_L}$$

$$\approx (1 + \chi_1) \left( \frac{1}{1 + \frac{C'_L}{C_{gs1}}} \right) z_1$$


$|p_1| > |z_1|$   
( $C'_L = 0$ )

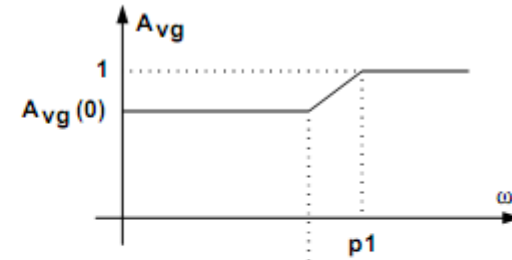

$|p_1| = |z_1|$

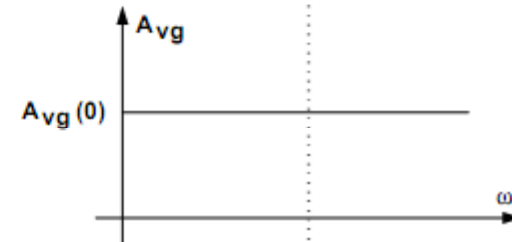

$|p_1| < |z_1|$

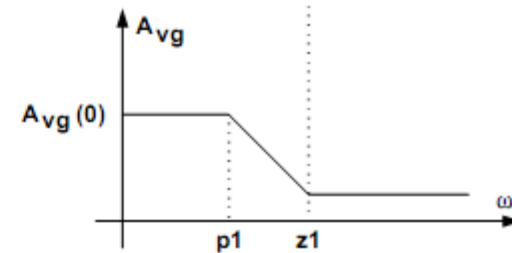

# Common-drain amplifier

The input admittance looking into the gate is

$$Y_g(s) = \frac{i_g}{V_g} = sC_{gs1}[1 - A_{vg}(s)] = \frac{sC_{gs1}(G'_L + sC'_L)}{g_{m1} + G'_L + s(C_{gs1} + C'_L)}$$


Define the capacitance looking into the gate as

$$Y_g(s) = sC_g(s)$$


$$C_g(j\omega) = C_{gs1}[1 - A_{vg}(j\omega)]$$

$$C_g(0) = C_{gs1}[1 - A_{vg}(0)]$$
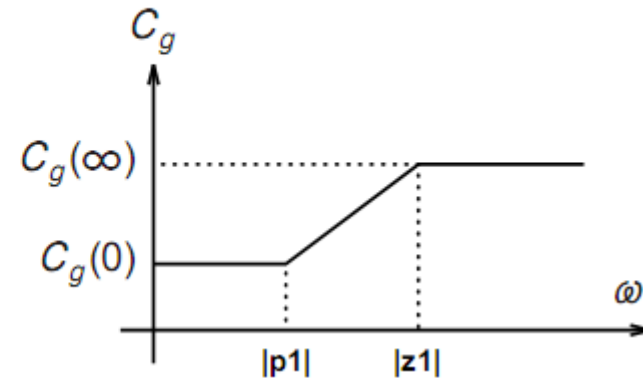
$$C_g(\infty) = C_{gs1}[1 - A_{vg}(\infty)] = \frac{C_{gs1}C'_L}{C_{gs1} + C'_L}$$



# Common-drain amplifier

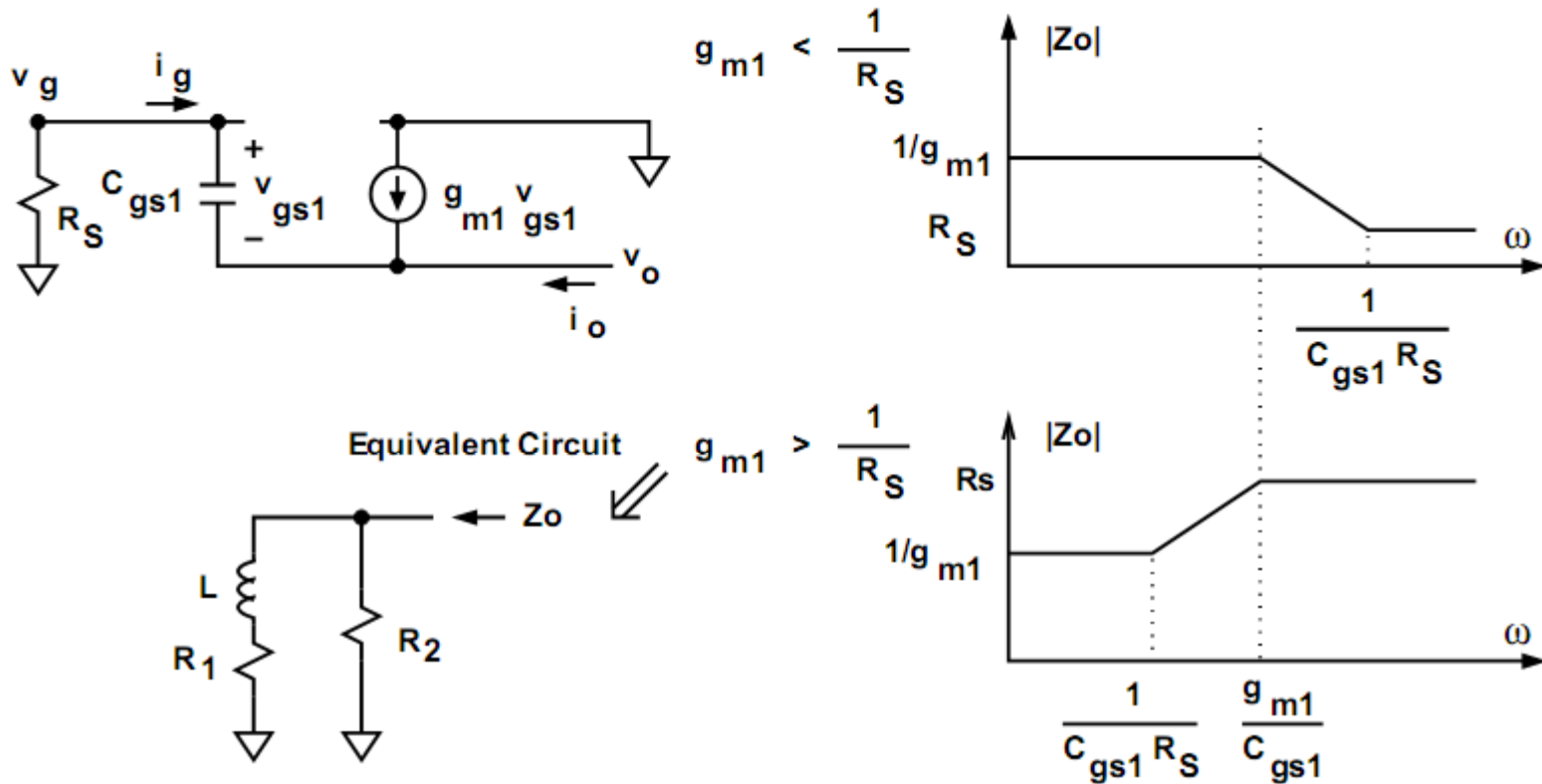

$$i_o = -(g_{m1} + sC_{gs1})(v_g - v_o) \quad G_S v_g + sC_{gs1}(v_g - v_o) = 0$$

# Common-drain amplifier

---

The output admittance is

$$Y_o(s) = \frac{1}{Z_o(s)} \equiv \frac{i_o}{v_o} = \frac{G_S(g_{m1} + sC_{gs1})}{G_S + sC_{gs1}} = G_S + \frac{G_S(g_{m1} - G_S)}{G_S + sC_{gs1}} = G_S + \frac{1}{\frac{1}{g_{m1} - G_S} + \frac{sC_{gs1}R_S}{g_{m1} - G_S}}$$

- Note that

$$Z_o(0) = \frac{1}{g_{m1}} \quad Z_o(\infty) = R_S$$

- The equivalent circuit is

$$R_1 = \frac{1}{g_{m1} - G_S} \quad R_2 = R_S \quad L = \frac{R_S C_{gs1}}{g_{m1} - G_S}$$

# Dominant pole approximation

---

The response of an amplifier has the form of

$$A(s) = A(0) \frac{N(s)}{D(s)} = A(0) \frac{1 + a_1 s + a_2 s^2 + \dots + a_m s^m}{1 + b_1 s + b_2 s^2 + \dots + b_n s^n} \approx \frac{A(0)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \dots \left(1 - \frac{s}{p_n}\right)}$$

If  $|p_1| \ll |p_2|, |p_3|, \dots, |p_n|$ , then  $p_1$  is a dominant pole. We have


$$b_1 = -\frac{1}{p_1} - \frac{1}{p_2} - \dots - \frac{1}{p_n} \approx -\frac{1}{p_1} = \left| \frac{1}{p_1} \right|$$

$$|A(j\omega)| = \frac{A(0)}{\sqrt{\left[1 + \left(\frac{\omega}{p_1}\right)^2\right] \left[1 + \left(\frac{\omega}{p_2}\right)^2\right] \dots \left[1 + \left(\frac{\omega}{p_n}\right)^2\right]}} \approx \frac{A(0)}{\sqrt{1 + \left(\frac{\omega}{p_1}\right)^2}}$$

$$\text{-3 dB Bandwidth} = \omega_{-3\text{dB}} \approx |p_1| \approx \frac{1}{b_1}$$

# Zero-value time constants

---

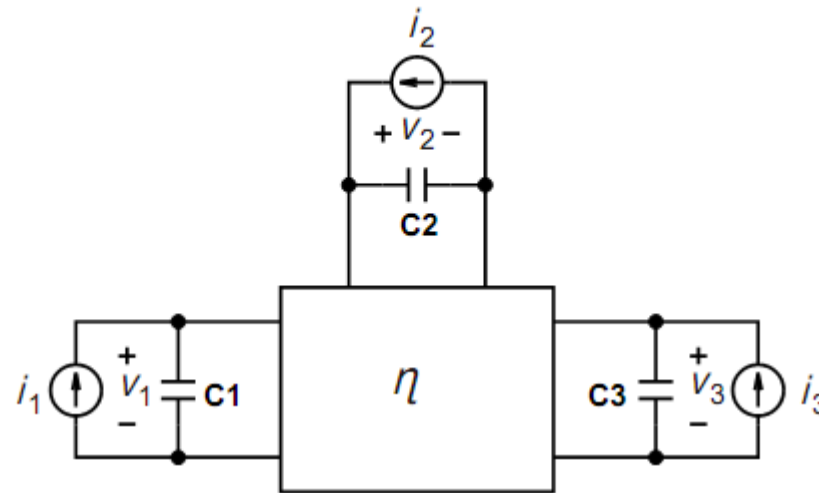


- $\eta$  is a linear active network without energy storage.
- The  $b_1$  in the denominator of the system function can be expressed as

$$b_1 = \sum T_0 = R_{10}C_1 + R_{20}C_2 + R_{30}C_3 + \dots$$

$R_{j0}$  is the driving point resistance seen by  $C_j$  with all capacitors equal to zero.

# Zero-value time constants

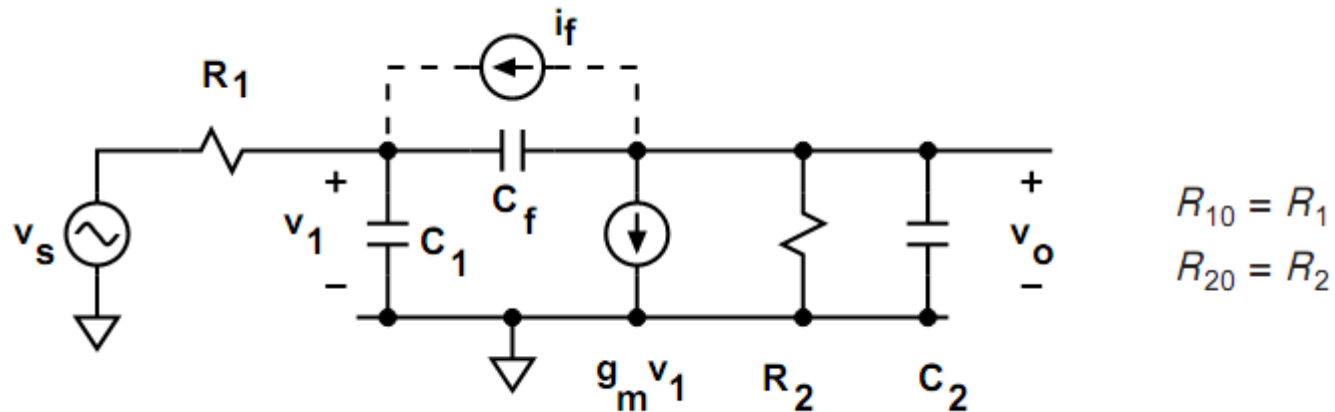

To determine  $R_{f0}$ , replace  $C_f$  with a current source  $i_f$ , then


$$v_1 = i_f R_1 \quad v_o = -(i_f + g_m v_1) R_2$$

$$R_{f0} = \frac{v_1 - v_o}{i_f} = R_1 + R_2 + g_m R_1 R_2 = R_1 \left( 1 + g_m R_2 + \frac{R_2}{R_1} \right)$$

We have

$$b_1 = \sum T_0 = R_1 C_1 + R_2 C_2 + (R_1 + R_2 + g_m R_1 R_2) C_f$$

# Cascode amplifiers

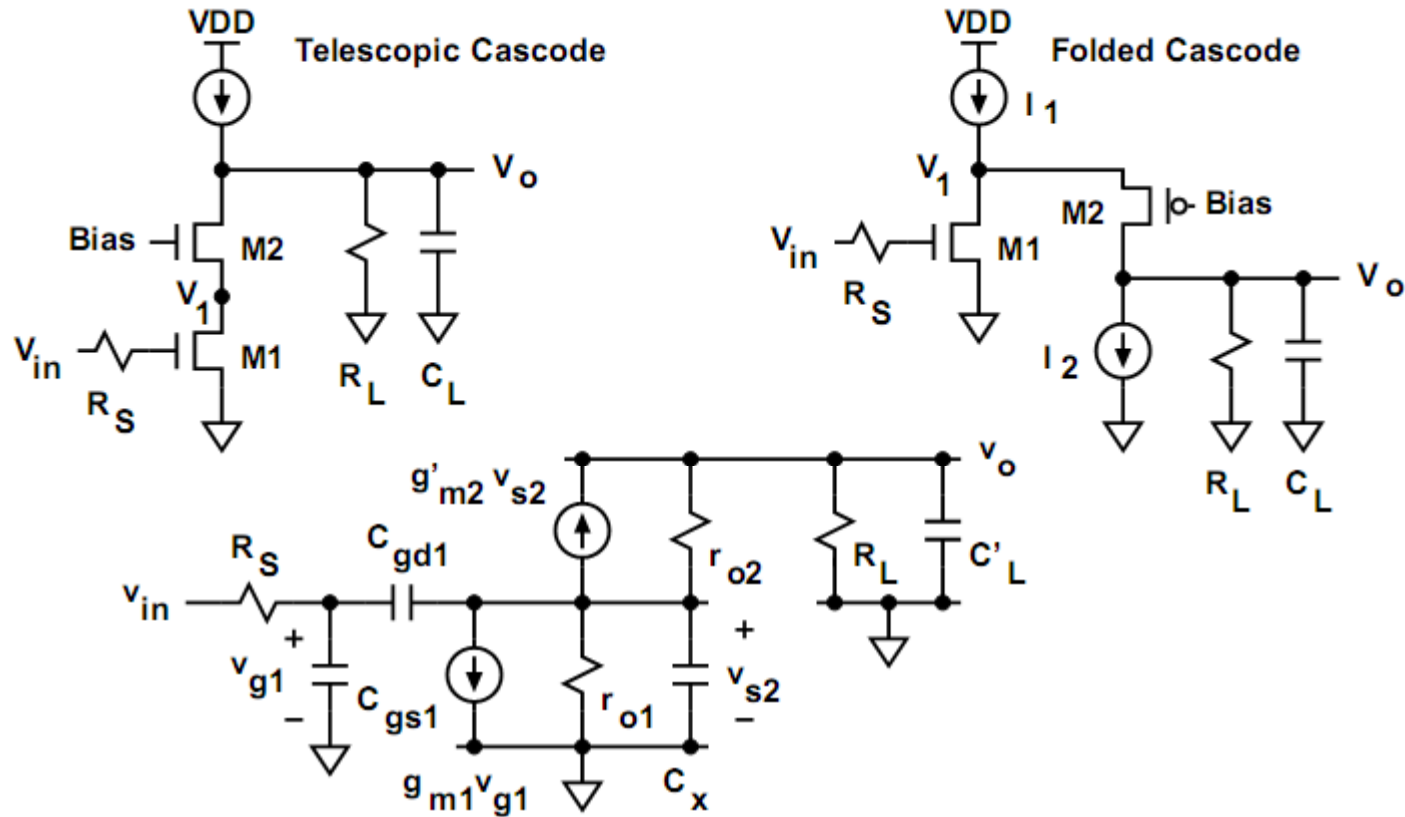

$$g'_{m2} = g_{m2} + g_{mb2} \quad C_x = C_{db1} + C'_{sb2} + C_{gs2} \quad C'_L = C_L + C_{db2} + C_{gd2}$$

# Cascode amplifiers

---

The output impedance looking into M2's drain is

$$R_{ot2} = r_{o1} + (g'_{m2}r_{o1} + 1)r_{o2} \approx g'_{m2}r_{o1}r_{o2}$$

The input admittance looking into M2's source is

$$G_{in2} \approx \frac{g'_{m2}}{g_{o2}/G_L + 1}$$

The overall voltage gain is

$$A_v = \frac{V_o}{V_{in}} \approx -\frac{g_{m1}}{g_{o1} + G_{in2}} \times \frac{g'_{m2}}{g_{o2} + G_L} = g_{m1} \times \frac{g'_{m2}r_{o1}r_{o2}R_L}{r_{o2} + g'_{m2}r_{o1}r_{o2} + R_L} \approx g_{m1} \times (R_{ot2} \parallel R_L)$$

- Let  $g_m = g_{m1} = g'_{m2}$ ,  $r_o = r_{o1} = r_{o2}$ , and  $g_m \gg g_o$ . If  $R_L = R_{ot2} = g_m r_o^2$ , then

$$G_{in2} \approx \frac{g_m}{g_o R_L + 1} \approx \frac{g_m}{g_m r_o + 1} \approx g_o \quad A_v \approx -\frac{g_m}{2g_o g_o + G_L} \approx -\frac{1}{2} \left( \frac{g_m}{g_o} \right)^2$$

# Cascode amplifiers

Using the zero-value time constant method, we have

$$R_{gs10} = R_S \quad R_{gd10} = R_S + R_{x0} + g_{m1}R_S R_{x0}$$

$$R_{x0} = r_{o1} \parallel R_{in2} \approx r_{o1} \parallel [(1/g'_{m2})(g_{o2}/G_L + 1)] \quad R_{L0} = R_L \parallel R_{ot2} \approx R_L \parallel (g'_{m2}r_{o1}r_{o2})$$

$$\sum T_0 = R_{gs10}C_{gs1} + R_{gd10}C_{gd1} + R_{x0}C_x + R_{L0}C_L \quad \omega_{-3dB} = 1 / \left( \sum T_0 \right)$$

- Let  $g_m = g_{m1} = g'_{m2}$ ,  $r_o = r_{o1} = r_{o2}$ ,  $g_m \gg g_o$ . If  $R_L = R_{ot2} = g_m r_o^2$  and  $R_S = r_o$ , then

$$R_{in2} \approx r_o \quad R_{x0} = \frac{r_o}{2} \quad R_{L0} \approx \frac{g_m r_o^2}{2} \quad R_{gd10} \approx R_S + \frac{r_o}{2} + \frac{g_m r_o R_S}{2} \approx \frac{g_m r_o^2}{2}$$

$$\Rightarrow \sum T_0 = R_S C_{gs1} + \frac{g_m r_o^2}{2} C_{gd1} + \frac{r_o}{2} C_x + \frac{g_m r_o^2}{2} C_L$$

- $R_{L0}C_L$  usually is the dominant term, unless  $R_S$  is very large.

# Cascode amplifiers

---

Let  $R_L = R_{ot2} = g'_{m2}r_{o1}r_{o2}$ , then

$$G_{in2} \approx \frac{g'_{m2}}{g_{o2}R_L + 1} \approx \frac{g'_{m2}}{g'_{m2}r_{o1} + 1} \approx g_{o1}$$

The dc gain is

$$A_V(0) \approx -\frac{g_{m1}}{g_{o1} + G_{in2}} \times \frac{g'_{m2}}{g_{o2} + G_L} \approx -\frac{1}{2} \cdot \frac{g_{m1}}{g_{o1}} \cdot \frac{g'_{m2}}{g_{o2}}$$

The dominant pole is

$$p_1 = -\frac{1}{R_{L0}C_L} \approx -\frac{2}{g'_{m2}r_{o1}r_{o2}C_L}$$

At frequencies where  $|p_1| \ll \omega \ll |p_2|$ ,

$$A_V(s) = \frac{A_V(0)}{1 - \frac{s}{p_1}} \approx \frac{A_V(0)}{-\frac{s}{p_1}} \approx -\frac{g_{m1}}{sC_L} = -\frac{\omega_u}{s} \quad \omega_u = A_V(0) \cdot p_1 = \frac{g_{m1}}{C_L}$$

# Cascode amplifiers

---

The second pole is approximately at

$$p_2 = -\frac{g_{o1} + Y_{in2}}{C_x}$$

$Y_{in2}$  is the resistance looking into the M2's source at high frequencies.

$$Y_{in2} = g'_{m2} - g_{o2} \left( \frac{v_o}{v_{s2}} - 1 \right)$$



- At frequencies  $\omega \gg (g_{o2} + G_L)/C_L$ ,

$$\frac{v_o}{v_{s2}} = \frac{g'_{m2} + g_{o2}}{g_{o2} + G_L + sC_L} \approx \frac{g'_{m2}}{sC_L} \Rightarrow Y_{in2} \approx g'_{m2} \left( 1 - \frac{g_{o2}}{sC_L} \right) + g_{o2} \approx g'_{m2}$$

$$p_2 \approx -\frac{g'_{m2}}{C_x} \approx -\frac{g_{m2}}{KC_{gs2}} \approx -\frac{\omega_T}{K}$$

where  $K$  is between 1 and 2 (usually closer to 1).

# Differential amplifier

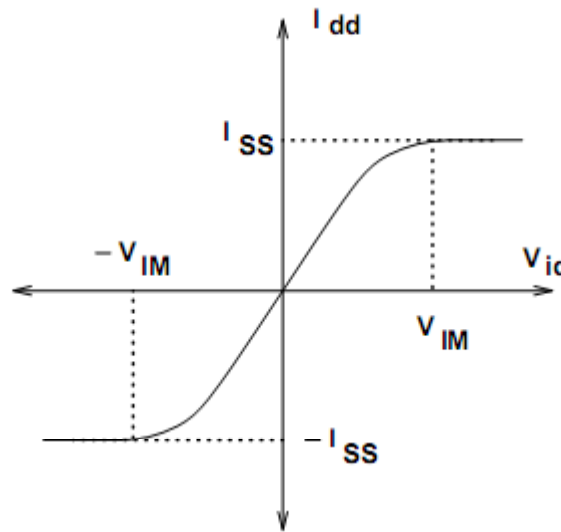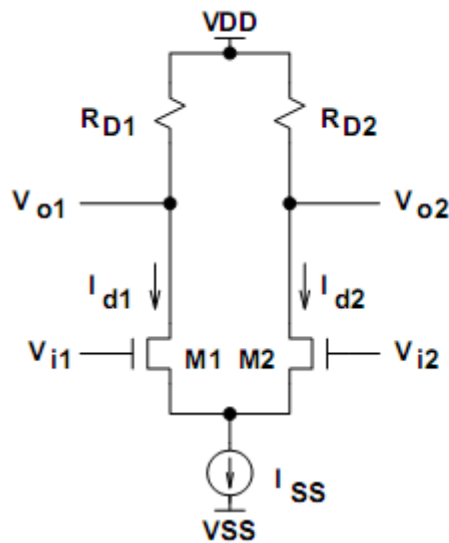

Assume

- $M1=M2$ .
- $R_{D1} = R_{D2} \equiv R_D$ .
- Neglect  $r_o$ .
- $R_{SS} \rightarrow \infty$ .

$$V_{id} \equiv V_{i1} - V_{i2} \quad I_{dd} \equiv I_{d1} - I_{d2} \quad V_{od} \equiv V_{o1} - V_{o2} = -I_{dd}R_D$$

Assume M1 and M2 are in the saturation region,

$$I_{d1} = \frac{1}{2}k(V_{gs1} - V_t)^2 \quad I_{d2} = \frac{1}{2}k(V_{gs2} - V_t)^2 \quad k = \mu C_{ox} \frac{W}{L}$$

# Differential amplifier – large-signal analysis

---

Summing currents at the common source node, we have

$$I_{d1} + I_{d2} = I_{SS} \quad \Rightarrow \quad I_{d1} = \frac{I_{SS}}{2} + \frac{I_{dd}}{2} \quad I_{d2} = \frac{I_{SS}}{2} - \frac{I_{dd}}{2}$$

The gate voltages can be written as

$$V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{K}} \quad V_{gs2} = V_t + \sqrt{\frac{2I_{d2}}{K}}$$

The differential input voltage is

$$V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}} = \sqrt{\frac{2}{k}} \left( \sqrt{I_{d1}} - \sqrt{I_{d2}} \right)$$

Squaring

$$V_{id}^2 = \frac{2}{k} \left[ I_{d1} + I_{d2} - 2\sqrt{I_{d1}I_{d2}} \right] = \frac{2}{k} \left[ I_{SS} - \sqrt{I_{SS}^2 - I_{dd}^2} \right]$$


# Differential amplifier – large-signal analysis

Rearrange, then we have

$$I_{dd} = \frac{k}{2} V_{id} \sqrt{\frac{4I_{SS}}{k} - V_{id}^2} \quad \text{and} \quad I_{d1} = \frac{I_{SS}}{2} + \frac{I_{dd}}{2} \quad I_{d2} = \frac{I_{SS}}{2} - \frac{I_{dd}}{2}$$

Define  $V_{IM}$  as the differential input voltage at which one of the MOST is turned off, i.e.,

$$I_{SS} = \frac{k}{2} V_{IM} \sqrt{\frac{4I_{SS}}{k} - V_{IM}^2} \Rightarrow V_{IM} = \sqrt{\frac{2I_{SS}}{k}} = \sqrt{2} (V_{ov1})|_{V_{id}=0} = \sqrt{2} (V_{ov2})|_{V_{id}=0}$$

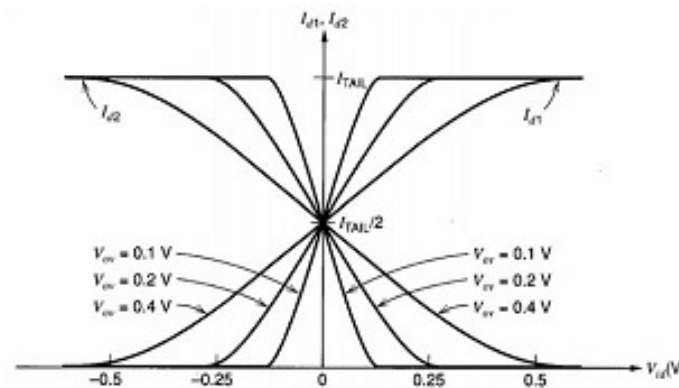

# Differential- and common-mode small-signal analysis

The small-signal performance of a differential amplifier can be separated into a differential mode and common mode analysis. This separation allows us to take advantage of the following simplifications.

Half-Circuit Concept:


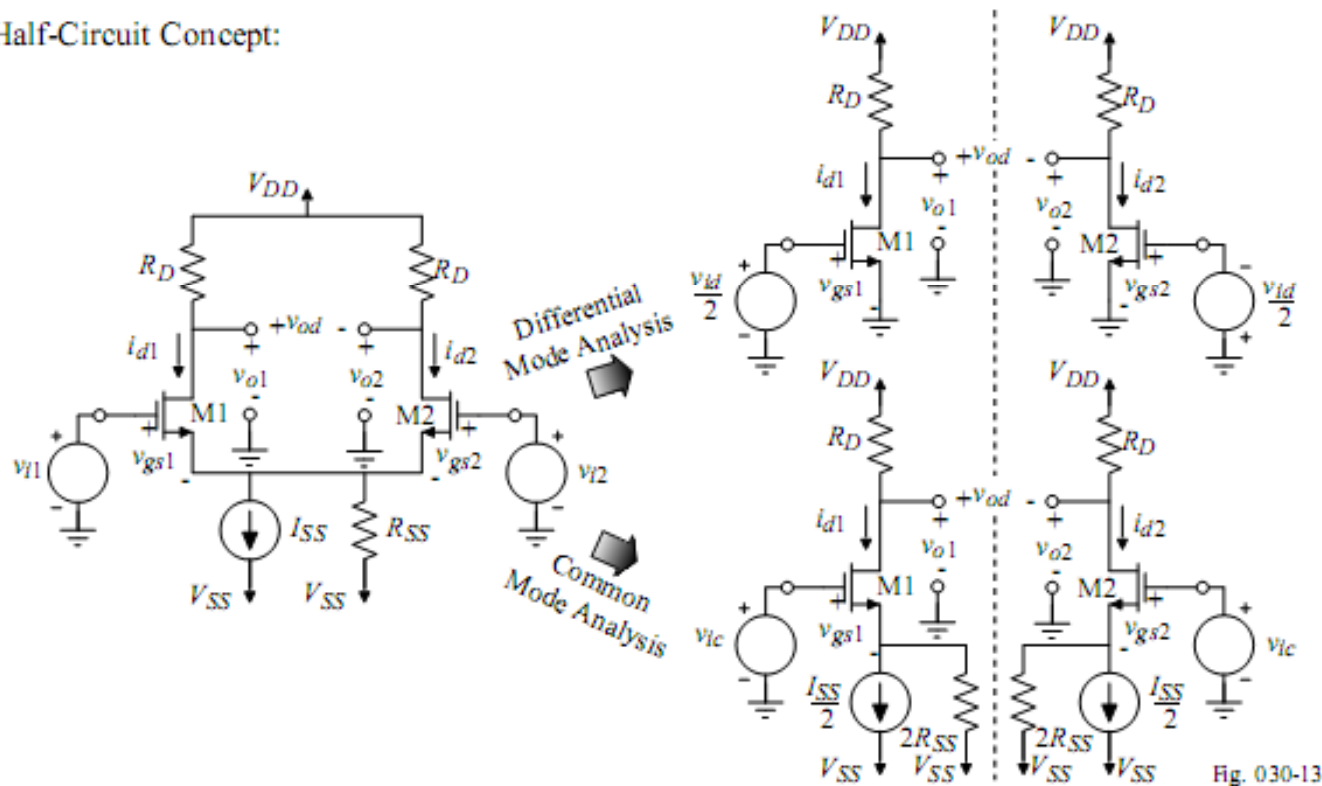


Fig. 030-13

Note: The half-circuit concept is valid as long as the resistance seen looking into each source is approximately the same.

# Differential-mode analysis

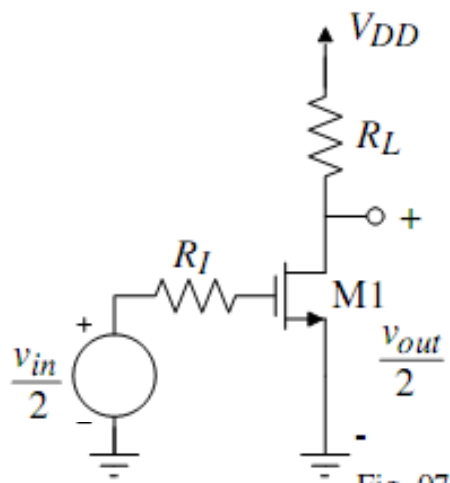

Small Signal Model:

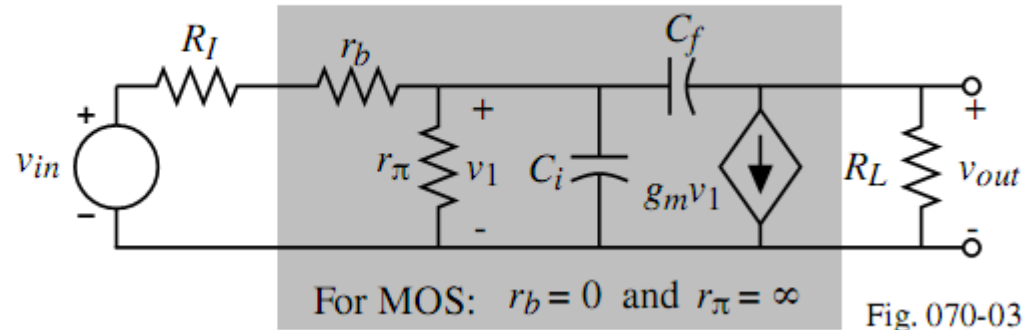


Fig. 070-03

Miller Approach:

Assume that  $R_L < (1/\omega C_f)$ , then  $v_{out} \approx -g_m R_L v_1$

Therefore, the small-signal model can be approximated as,

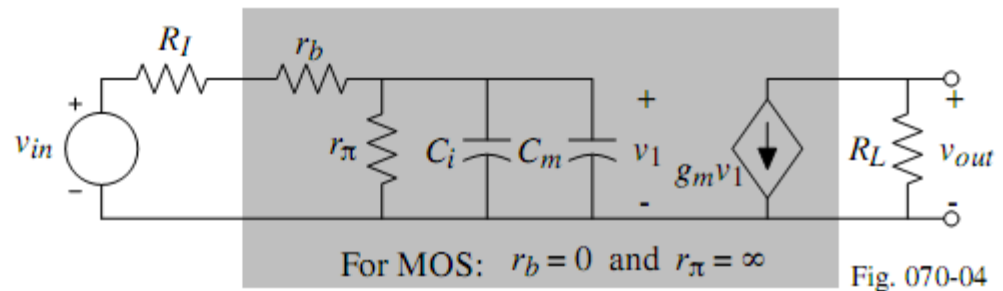


Fig. 070-04

where

$$C_m = C_f(1 + g_m R_L)$$

# Differential-mode analysis

The small-signal analysis of the previous circuit defining  $C_t = C_i + C_m$  is,

$$\frac{v_{out}}{v_{in}} = \left( \frac{v_{out}}{v_1} \right) \left( \frac{v_1}{v_{in}} \right) = (-g_m R_L) \left( \frac{\frac{r_\pi}{1 + r_\pi C_t s}}{\frac{r_\pi}{1 + r_\pi C_t s} + R_I + r_b} \right) = -g_m R_L \left( \frac{r_\pi}{r_\pi + R_I + r_b} \right) \left( \frac{1}{1 + \frac{s r_\pi C_t (R_I + r_b)}{r_\pi + R_I + r_b}} \right)$$

Therefore we see that the gain ( $K$ ), pole ( $p_1$ ), and -3dB frequency ( $\omega_{-3dB}$ ) is given as,

	$K$	$p_1$	$\omega_{-3dB}$
BJT	$-g_m R_L \left( \frac{r_\pi}{r_\pi + R_I + r_b} \right)$	$\frac{r_\pi + R_I + r_b}{-r_\pi C_t (R_I + r_b)}$	$\frac{r_\pi + R_I + r_b}{r_\pi C_t (R_I + r_b)}$
MOS	$-g_m R_L$	$\frac{1}{-C_t R_I}$	$\frac{1}{C_t R_I}$

# Common-mode analysis

Assumptions: Tail capacitance is dominant and self-resistance is negligible.

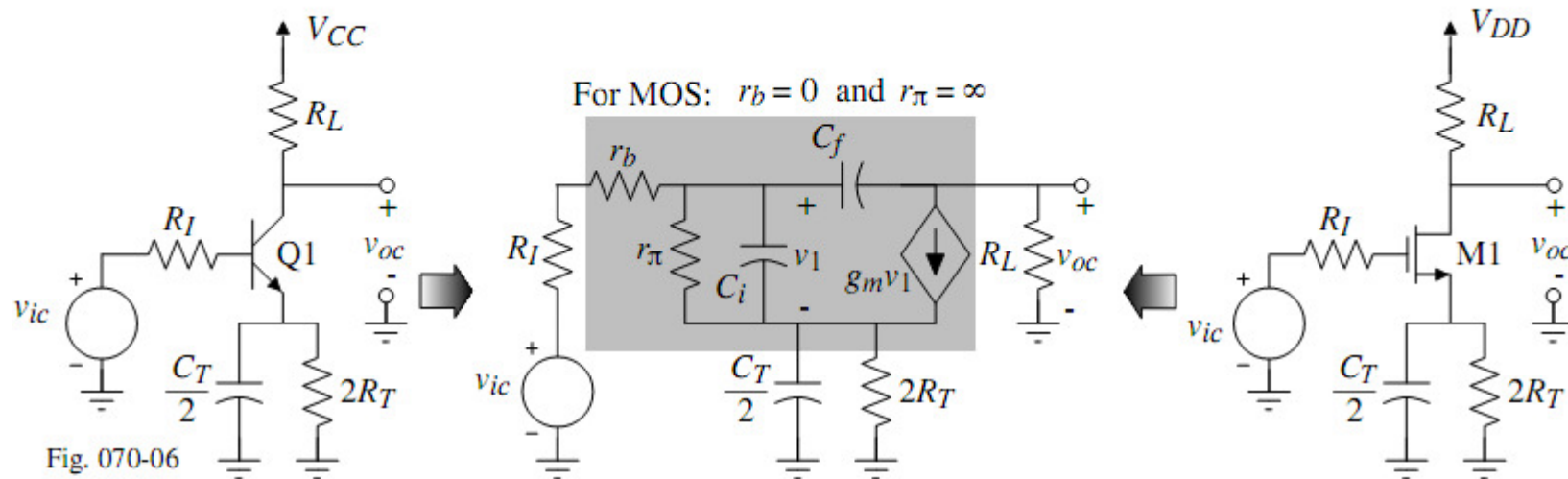



Fig. 070-06

$$\therefore A_{cm} = \frac{v_{oc}}{v_{ic}} \approx -\frac{R_L}{Z_T} \quad \text{where} \quad Z_T = \frac{2R_T}{1+sR_T C_T} \quad \Rightarrow \quad A_{cm} = \frac{v_{oc}}{v_{ic}} \approx -\frac{R_L}{2R_T}(1+sR_T C_T)$$


This zero at  $\omega = 1/R_T C_T$  causes the CM gain to increase, resulting in a CMRR decrease.

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{\left( \frac{g_m 2R_T r_\pi}{r_\pi + R_I + r_b} \right) \left( \frac{1}{1 + \frac{s r_\pi C_t (R_I + r_b)}{r_\pi + R_I + r_b}} \right)}{(1+sR_T C_T)} = \left( \frac{g_m 2R_T r_\pi}{r_\pi + R_I + r_b} \right) \left( \frac{1}{(1+s/\omega_T)(1+s/p_1)} \right)$$

# CMRR frequency response

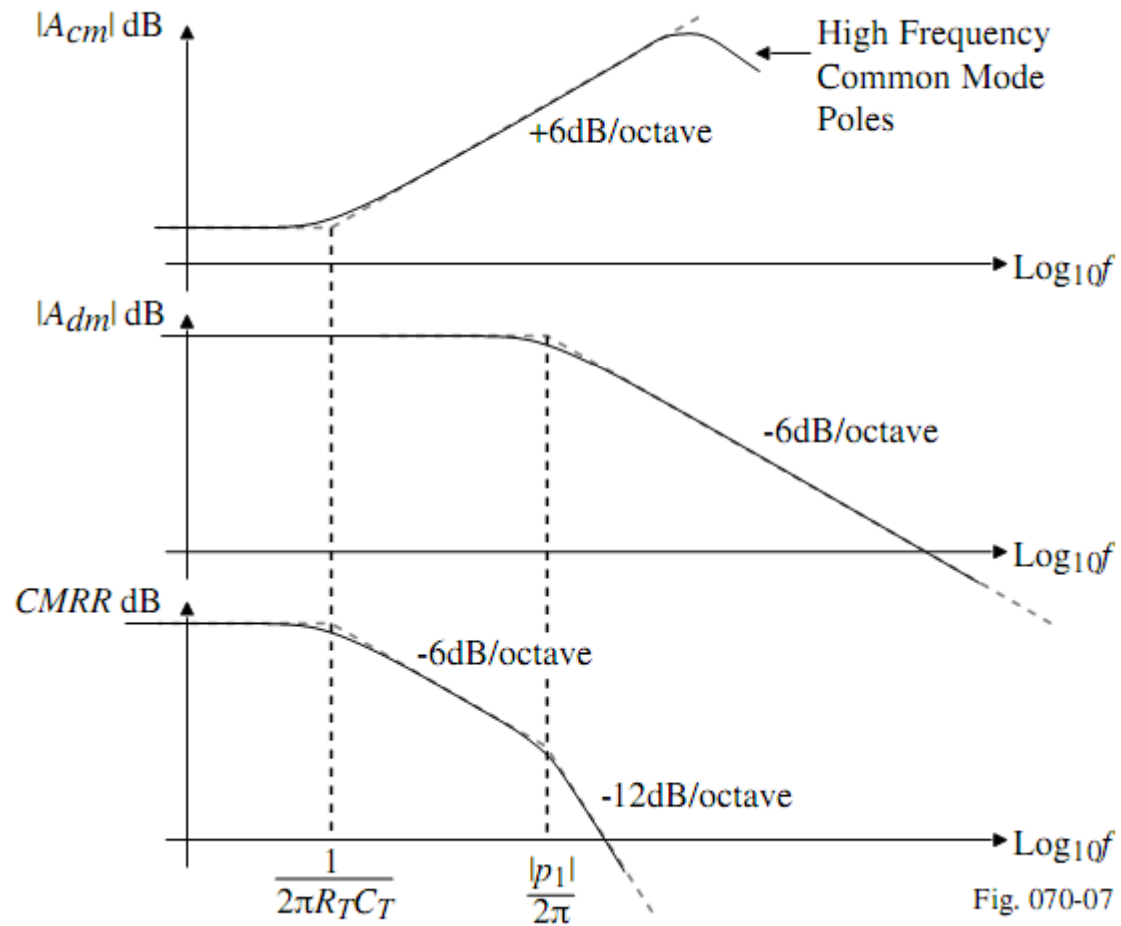

# Current-mirrors

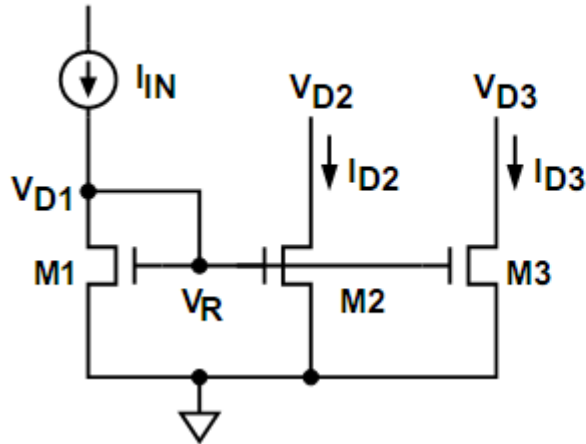

$$k' = \mu_n C_{ox}$$

$$I_{IN} = \frac{1}{2} k' \left( \frac{W}{L} \right)_1 (V_R - V_{t1})^2 (1 + \lambda_1 V_{D1})$$

$$I_{D2} = \frac{1}{2} k' \left( \frac{W}{L} \right)_2 (V_R - V_{t2})^2 (1 + \lambda_2 V_{D2})$$


$$I_{D3} = \frac{1}{2} k' \left( \frac{W}{L} \right)_3 (V_R - V_{t3})^2 (1 + \lambda_3 V_{D3})$$

Let  $V_{t1} = V_{t2} = V_t$  and  $\lambda_1 = \lambda_2 = \lambda$ , then

$$I_{D2} = I_{IN} \cdot \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1 + \lambda V_{D2}}{1 + \lambda V_{D1}} = I_{IN} \cdot \frac{(W/L)_2}{(W/L)_1} \cdot (1 + \epsilon) \quad \epsilon \approx \lambda(V_{D2} - V_{D1}) = \frac{V_{D2} - V_{D1}}{V_A}$$

$$R_{o2} = r_{o2} = \frac{1}{\lambda_2 I_{D2}} \quad V_{o2(min)} = V_{ov2} \approx V_{ov1} \approx \sqrt{\frac{2I_{IN}}{k'(W/L)_1}} \quad V_{DD(min)} = V_{GS1} = V_t + V_{ov1}$$

# Cascode current mirror

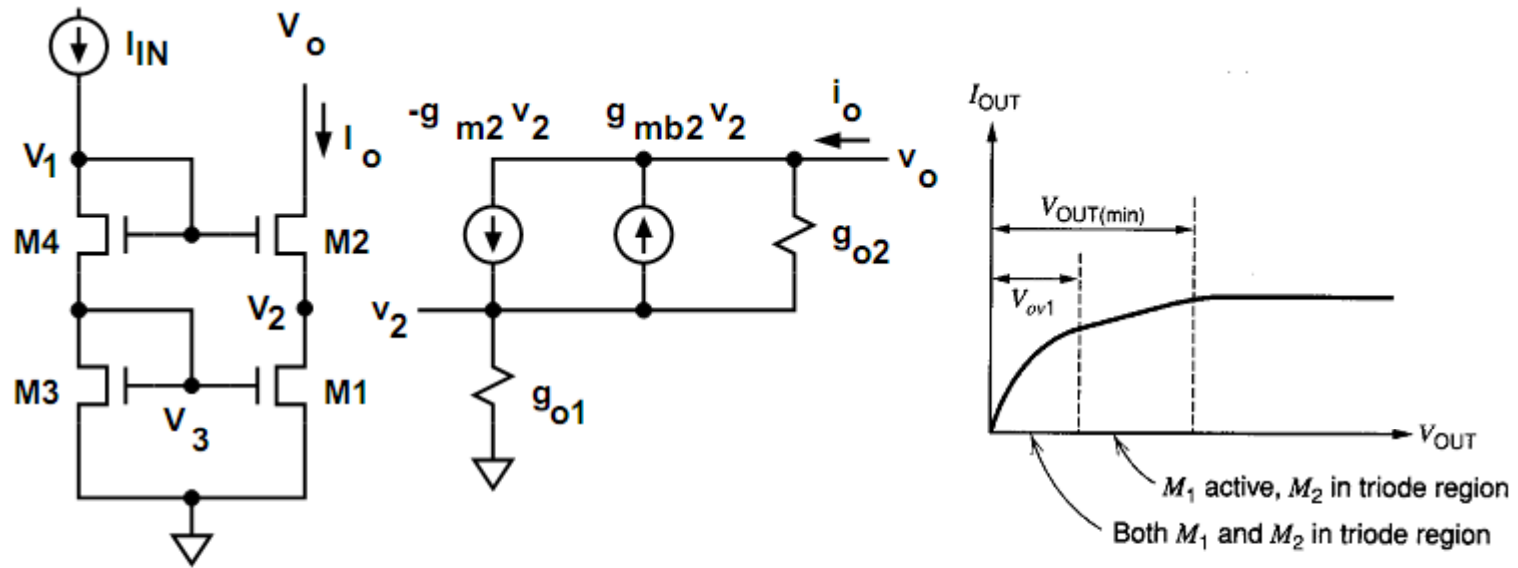


$$R_o = r_{o1}r_{o2}(g_{m2} + g_{mb2} + g_{o1} + g_{o2}) \approx r_{o1}r_{o2}g_{m2}(1 + \chi_2)$$

$$V_{o(min)} = V_{DS1} + V_{DSAT2} = V_{t3} + V_{ov3} + V_{ov2}$$

$$V_{DD(min)} = V_{GS3} + V_{GS4} = V_{t3} + V_{t4} + V_{ov3} + V_{ov4}$$

$$\epsilon \approx 0$$

# High-swing cascode current mirror

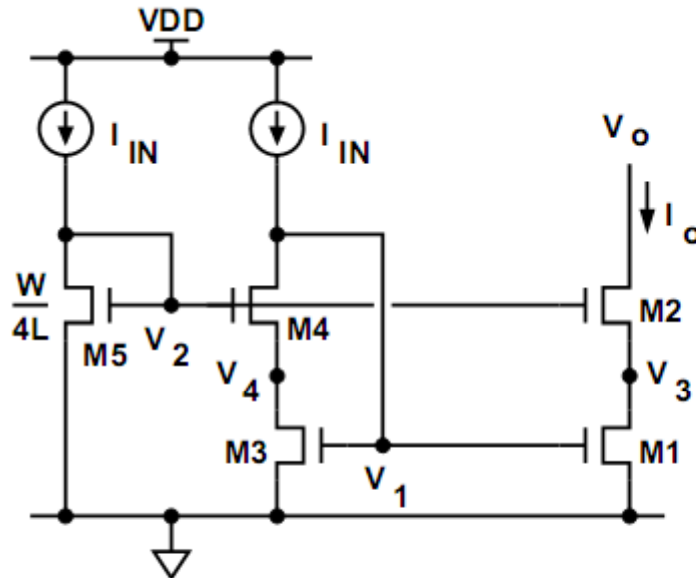

$$V_1 = V_t + V_{ov}$$

$$V_2 = V_t + 2V_{ov}$$

$$V_3 = V_{ov}$$

$$V_4 = V_{ov}$$


$$V_{o(min)} = V_{DS1} + V_{DSAT2} = 2V_{ov}$$

$$V_{DD(min)} = V_2 = V_t + 2V_{ov}$$

$$\epsilon = 0$$

- In practice, select  $(W/L)_5 < (1/4)(W/L)$  due to body effect and design margin.
- To bias M2 and M4 in the active region, want  $V_2 - V_1 < V_t \Rightarrow V_{ov} < V_t$ .

# Common-source with current source load

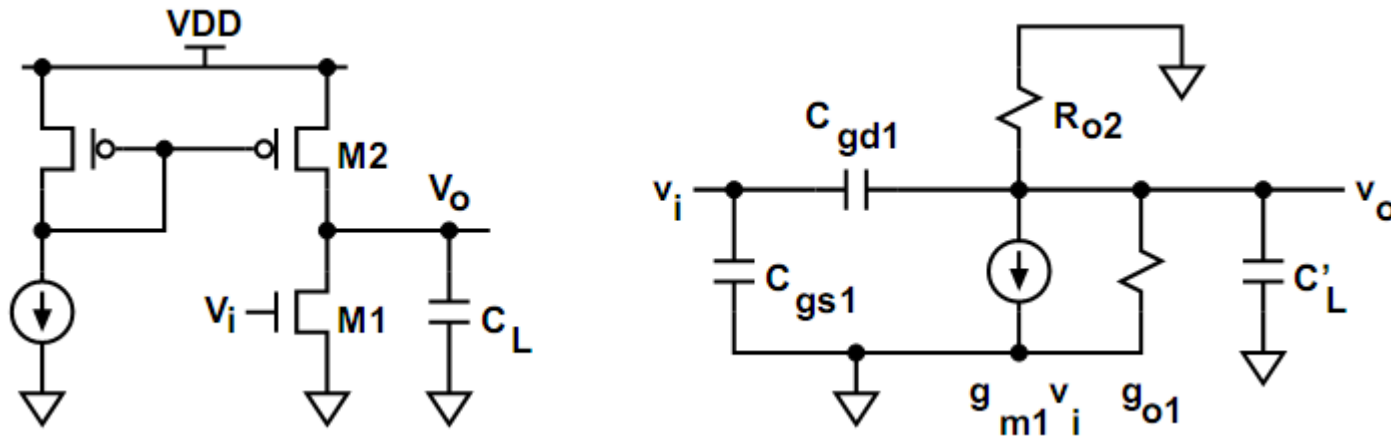

$$G'_L = g_{o1} + G_{o2} \quad C'_L = C_L + C_{o2}$$

- The  $V_o$  range in normal operation is between  $V_{DSAT1}$  and  $V_{DD} - V_{o2(min)}$ .

# Common-source amplifier with active loads

