

# Current and Voltage References

Apinunt Thanachayanont

# Sensitivity and temperature coefficient

---

- The *sensitivity* of a parameter  $y$  to a second one  $x$  is defined as

$$S_x^y \equiv \frac{\left(\frac{\Delta y}{y}\right)}{\left(\frac{\Delta x}{x}\right)} = \frac{x}{y} \cdot \frac{\partial y}{\partial x}$$

- The variation of a parameter  $y$  that results from changes in temperature is usually characterized by its *fractional temperature coefficient*, which is defined as the fractional change per degree centigrade change in temperature.

$$TC_y \equiv \frac{\left(\frac{\Delta y}{y}\right)}{\Delta T} = \frac{1}{y} \cdot \frac{\partial y}{\partial T}$$

$$TC_F = \frac{1}{V_{REF}} \left( \frac{\partial V_{REF}}{\partial T} \right) = \frac{1}{T} S_T^{V_{REF}} \text{ parts per million per } ^\circ\text{C or ppm}/^\circ\text{C}$$

# Temperature dependence

---

Temperature dependence of PN junctions:

$$\left. \begin{aligned} i &\approx I_s \exp\left(\frac{v}{V_t}\right) \\ I_s &= KT^3 \exp\left(\frac{-V_{GO}}{V_t}\right) \end{aligned} \right\} \frac{1}{I_s} \left(\frac{\partial I_s}{\partial T}\right) = \frac{\partial(\ln I_s)}{\partial T} = \frac{3}{T} + \frac{V_{GO}}{TV_t} \approx \frac{V_{GO}}{TV_t}$$

$$\frac{dv_{BE}}{dT} \approx \frac{V_{BE} - V_{GO}}{T} = -2\text{mV}/^\circ\text{C} \text{ at room temperature}$$

( $V_{GO} = 1.205 \text{ V}$  at room temperature and is called the bandgap voltage)



Temperature dependence of MOSFET in strong inversion:

$$\left. \begin{aligned} \frac{dv_{GS}}{dT} &= \frac{dV_T}{dT} + \sqrt{\frac{2L}{WC_{ox}}} \frac{d}{dT} \left( \sqrt{\frac{i_D}{\mu_o}} \right) \\ \mu_o &= KT^{-1.5} \\ V_T(T) &= V_T(T_o) - \alpha(T - T_o) \end{aligned} \right\} \frac{dv_{GS}}{dT} \approx -\alpha \approx -2.3 \frac{\text{mV}}{^\circ\text{C}}$$

Resistors:

$$(1/R)(dR/dT) \text{ ppm}/^\circ\text{C}$$

# Simple current source

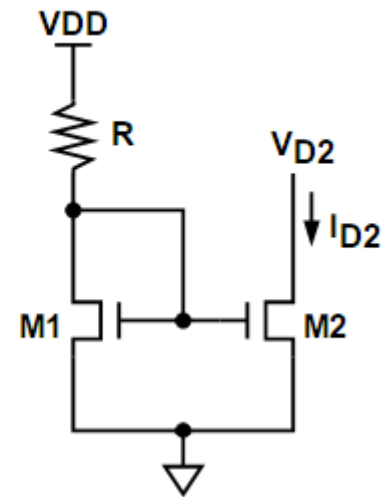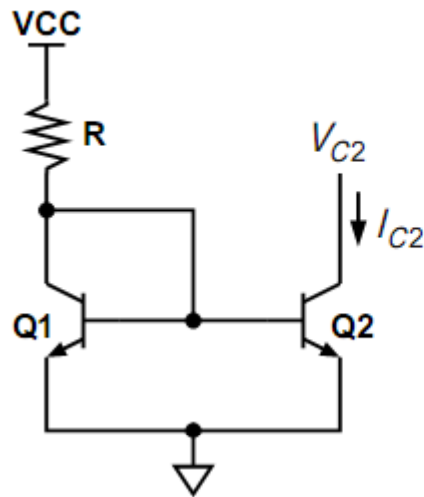


$$I_{C2} \approx I_{C1} \approx \frac{V_{CC} - V_{BE1(on)}}{R} \approx \frac{V_{CC}}{R}$$

$$S_{V_{CC}}^{I_{C2}} = \frac{V_{CC}}{I_{C2}} \cdot \frac{\partial I_{C2}}{\partial V_{CC}} = \frac{V_{CC}}{V_{CC}/R} \cdot \frac{\partial}{\partial V_{CC}} \left( \frac{V_{CC}}{R} \right) = R \cdot \left( \frac{1}{R} \right) = 1$$

$$\frac{\partial I_{C2}}{\partial T} = \frac{1}{R} \frac{\partial V_{CC}}{\partial T} - \frac{V_{CC}}{R^2} \frac{\partial R}{\partial T} = I_{C2} \left( \frac{1}{V_{CC}} \frac{\partial V_{CC}}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} \right) \Rightarrow TC_{I_{C2}} = TC_{V_{CC}} - TC_R$$

# Widlar current source

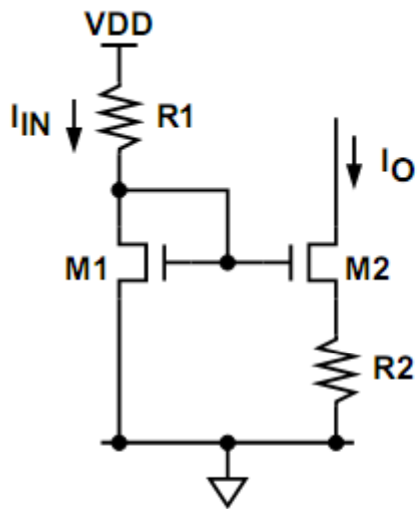

Let  $V_A \rightarrow \infty$  and  $\gamma \rightarrow 0$ ,

$$I_{IN} = \frac{V_{DD} - V_{ov1} - V_t}{R_1} = \frac{1}{2} k' \left( \frac{W}{L} \right)_1 V_{ov1}^2 \quad V_{ov1} = \sqrt{\frac{2I_{IN}}{k'(W/L)_1}}$$

$$V_{ov1} = V_{ov2} + I_O R_2 \Rightarrow I_O R_2 + \sqrt{\frac{2I_O}{k'(W/L)_2}} - V_{ov1} = 0$$

$$\sqrt{I_O} = \frac{1}{2R_2} \left( -\sqrt{\frac{2}{k'(W/L)_2}} + \sqrt{\frac{2}{k'(W/L)_2} + 4R_2 V_{ov1}} \right)$$

$$\frac{1}{2\sqrt{I_O}} \frac{\partial I_O}{\partial V_{DD}} = \frac{1}{4R_2} \frac{1}{\sqrt{\frac{2}{k'(W/L)_2} + 4R_2 V_{ov1}}} 4R_2 \frac{\partial V_{ov1}}{\partial V_{DD}} \quad \frac{\partial V_{ov1}}{\partial V_{DD}} = \sqrt{\frac{2}{k'(W/L)_1}} \frac{1}{2\sqrt{I_{IN}}} \frac{\partial I_{IN}}{\partial V_{DD}}$$

$$S_{V_{DD}}^{I_O} = \frac{V_{ov1}}{\sqrt{V_{ov2}^2 + 4I_O R_2 V_{ov1}}} S_{V_{DD}}^{I_{IN}} \approx \frac{V_{ov1}}{\sqrt{4V_{ov1}^2}} S_{V_{DD}}^{I_{IN}} = \frac{1}{2} S_{V_{DD}}^{I_{IN}}$$

# Threshold referenced current source

Circuit:

Operation:

$$I_{OUT} = \frac{V_{GS1}}{R_2} = \frac{V_T + \sqrt{\frac{2I_{IN}}{K'(W_1/L_1)}}}{R_2}$$

$$\approx \frac{V_T}{R_2} \text{ if } V_T > V_{ON1}$$

The sensitivity of  $I_{OUT}$  with respect to  $V_{DD}$  is

$$S_{V_{DD}}^{I_{OUT}} = \left( \frac{V_{ON1}}{I_{OUT}R_2} \right) S_{V_{DD}}^{I_{IN}} = \left( \frac{V_{ON1}}{2V_{GS1}} \right) S_{V_{DD}}^{I_{IN}}$$

For example, if  $V_T = 1V$ ,  $V_{ON1} = 0.1V$  and  $S_{V_{DD}}^{I_{IN}} \approx 1$ , then

$$S_{V_{DD}}^{I_{OUT}} = \left( \frac{0.1}{2 \cdot 1.1} \right) = 0.045$$

Therefore, if  $V_{DD}$  changes by 10%,  $I_{REF}$  or  $I_{OUT}$  changes by 0.45%.


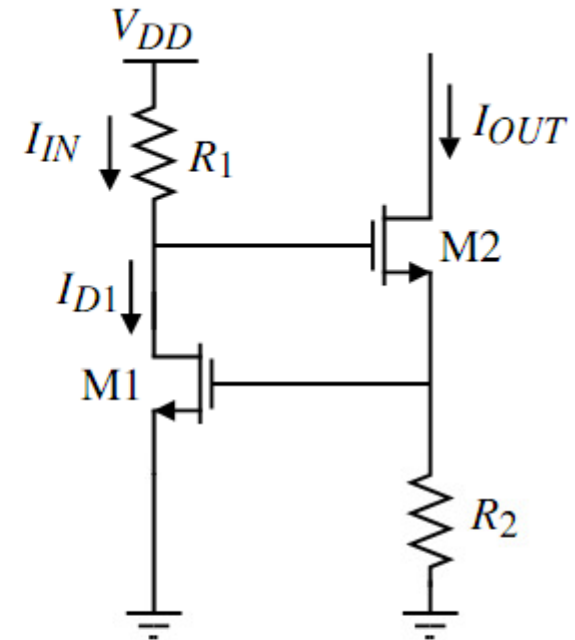
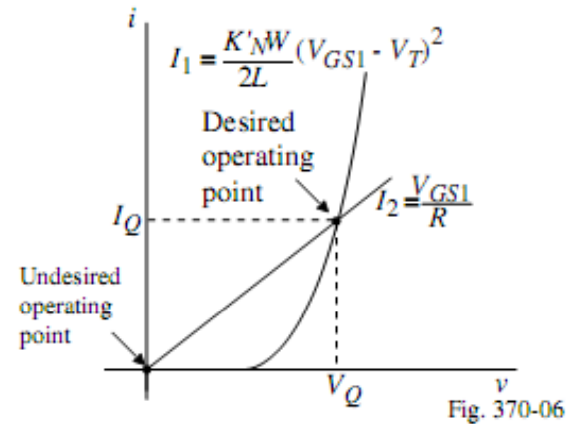


Fig. 360-1

# Bootstrapped current source

- ▶ Very good power supply independent!

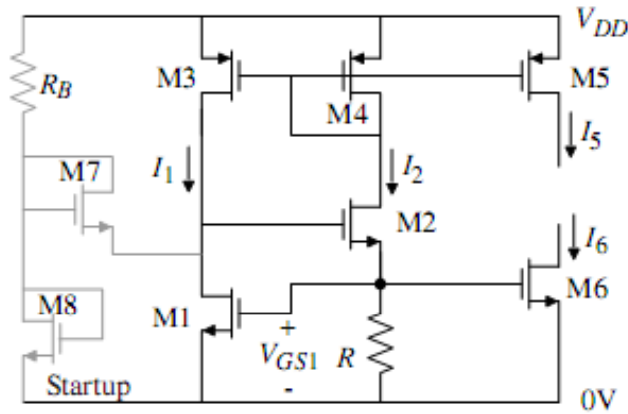

Principle:

If  $M3 = M4$ , then  $I_1 \approx I_2$ . However, the  $M1$ - $R$  loop gives  $V_{GS1} = V_{T1} + \sqrt{\frac{2I_1}{K_{N'}(W_1/L_1)}}$

Solving these two equations gives  $I_2 = \frac{V_{GS1}}{R} = \frac{V_{T1}}{R} + \left(\frac{1}{R}\right) \sqrt{\frac{2I_1}{K_{N'}(W_1/L_1)}}$

The output current,  $I_{out} = I_1 = I_2$  can be solved as  $I_{out} = \frac{V_{T1}}{R} + \frac{1}{\beta_1 R^2} + \frac{1}{R} \sqrt{\frac{2V_{T1}}{\beta_1 R} + \frac{1}{(\beta_1 R)^2}}$

# Constant Gm biasing

## Technique to Make $g_m$ Dependent on a Resistor

Consider the following circuit with all transistors having a  $W/L = 10$ . This is a bootstrapped reference which creates a  $V_{bias}$  independent of  $V_{DD}$ . The two key equations are:

$$I_3 = I_4 \Rightarrow I_1 = I_2$$

and

$$V_{GS1} = V_{GS2} + I_2 R$$

Solving for  $I_2$  gives:

$$I_2 = \frac{V_{GS1} - V_{GS2}}{R} = \frac{1}{R} \left( \sqrt{\frac{2I_1}{\beta_1}} - \sqrt{\frac{2I_2}{\beta_2}} \right) = \frac{\sqrt{2I_1}}{R\sqrt{\beta_1}} \left( 1 - \frac{1}{2} \right)$$

$$\therefore \sqrt{I_2} = \frac{1}{R\sqrt{2\beta_1}} \Rightarrow I_2 = I_1 = \frac{1}{2\beta_1 R^2} = \frac{1}{2 \cdot 110 \times 10^{-6} \cdot 10 \cdot 25 \times 10^6} = 18.18 \mu A$$


Now,  $V_{bias}$  can be written as

$$V_{bias} = V_{GS1} = \sqrt{\frac{2I_2}{\beta_1}} + V_{TN} = \frac{1}{\beta_1 R} + V_{TN} = \frac{1}{110 \times 10^{-6} \cdot 10 \cdot 5 \times 10^3} + 0.7 = 0.1818 + 0.7 = 0.8818 V$$


Any transistor with  $V_{GS} = V_{bias}$  will have a current flow that is given by  $1/2\beta R^2$ .

Therefore, 
$$g_m = \sqrt{2I\beta} = \sqrt{\frac{2\beta}{2\beta R^2}} = \frac{1}{R} \Rightarrow \boxed{g_m = \frac{1}{R}}$$

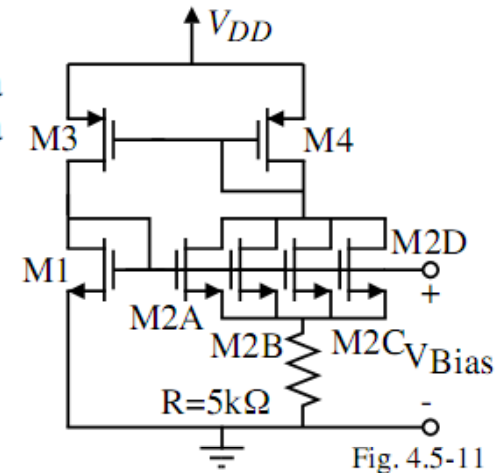
(This means that the temperature dependence of  $g_m$  will be that of  $1/R$  which can be used to achieve temperature controlled performance.)



# Bootstrapped current sources

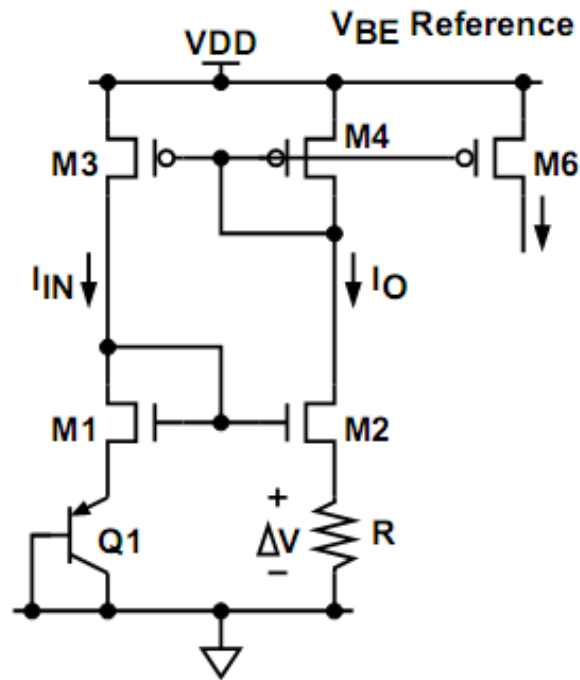

$$\Delta V = V_{BE1}$$

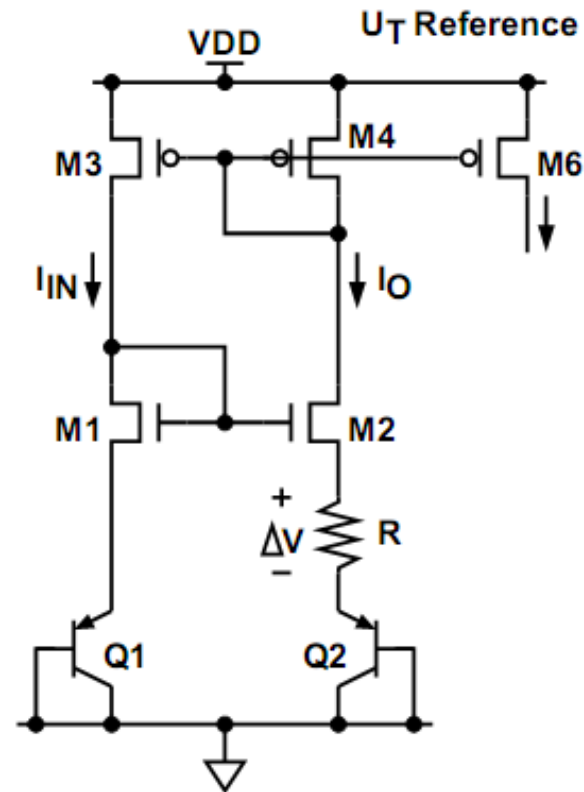


$$\Delta V = U_T \ln \left( \frac{I_{S2}}{I_{S1}} \cdot \frac{(W/L)_3}{(W/L)_4} \right)$$

Also known as PTAT current source

# Bandgap reference

---

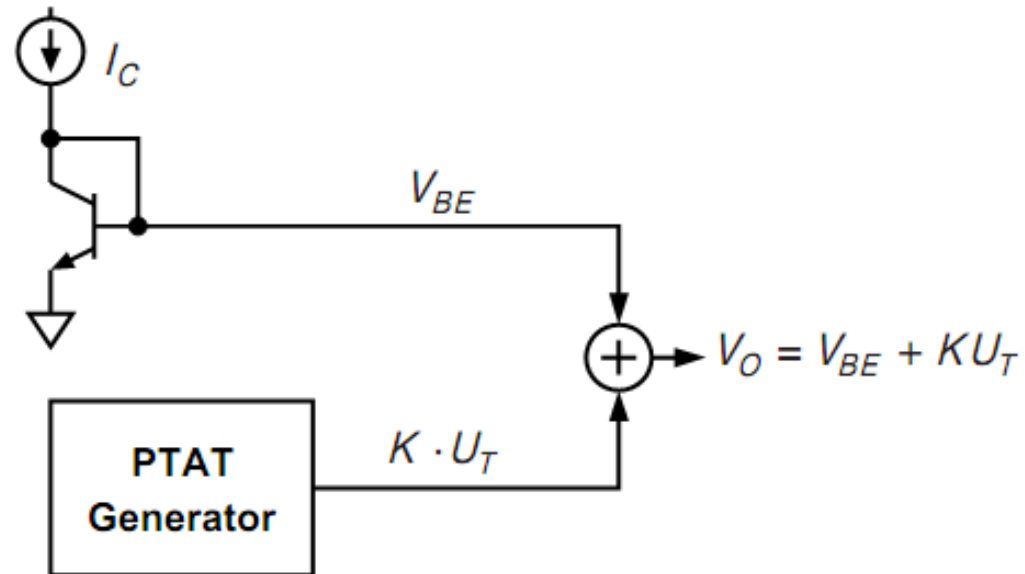

- $U_T = kT/q = 26 \text{ mV}$  at  $T = 300^\circ\text{K}$ .  $\partial U_T / \partial T = k/q = 0.087 \text{ mV}/^\circ\text{C}$ .
- $V_{BE} = 600 \text{ mV}$  at  $T = 300^\circ\text{K}$ .  $\partial V_{BE} / \partial T \approx -2 \text{ mV}/^\circ\text{C}$ .
- Want  $K = 23$  so that  $\partial V_O / \partial T = 0$  at  $300^\circ\text{K}$  and  $V_O \approx 1.2 \text{ V}$ .

# Bandgap reference

---

For a BJT biased in the forward-active region, we have

$$V_{BE} = V_{G0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \frac{T}{T_0} + mU_T \ln \left(\frac{T_0}{T}\right) + U_T \ln \left(\frac{J_C}{J_{C0}}\right) \quad U_T = \frac{kT}{q}$$

$V_{G0}$  Bandgap voltage of Si extrapolated to 0°K ( $\approx 1.206$  V)

$k$  Boltzmann's constant

$m$  Constant ( $\approx 2.3$ )

$T_0$  Reference temperature

$J_C$  Collector current density ( $= I_C/A_E$ )

$J_{C0}$  Collector current density at  $T_0$

Let

$$V_O = V_{BE} + KU_T \quad \text{and} \quad \frac{J_C}{J_{C0}} = \left(\frac{T}{T_0}\right)^\alpha$$

We have

$$V_O = V_{G0} + \frac{T}{T_0}(V_{BE0} - V_{G0}) + (m - \alpha)U_T \ln \left(\frac{T_0}{T}\right) + K \cdot U_T$$

# Bandgap reference

---

Then

$$\frac{\partial V_O}{\partial T} = \frac{1}{T_0}(V_{BE0} - V_{G0}) + (m - \alpha)\frac{k}{q} \left[ \ln\left(\frac{T_0}{T}\right) - 1 \right] + K \cdot \frac{k}{q}$$

Set  $\partial V_O/\partial T = 0$  at  $T = T_0$ , we obtain

$$K = \frac{1}{U_{T0}} \cdot [V_{G0} + (m - \alpha)U_{T0} - V_{BE0}] \quad U_{T0} = \frac{kT_0}{q}$$

$$V_O = V_{G0} + U_T(m - \alpha) \left[ 1 + \ln\left(\frac{T_0}{T}\right) \right] \quad \frac{\partial V_O}{\partial T} = \frac{k}{q}(m - \alpha) \ln\left(\frac{T_0}{T}\right)$$


- At  $T = T_0$ ,

$$V_O = V_{G0} + U_{T0}(m - \alpha) \quad \frac{\partial V_O}{\partial T} = 0$$


- If  $T_0 = 300^\circ\text{K}$  and  $\alpha = 1$ , then,

$$K = \frac{1.24 - V_{BE0}}{0.0258} \quad \text{and} \quad V_O = 1.24 \text{ V} \quad \text{at } T = T_0$$

# Bandgap reference voltage vs. Temp.

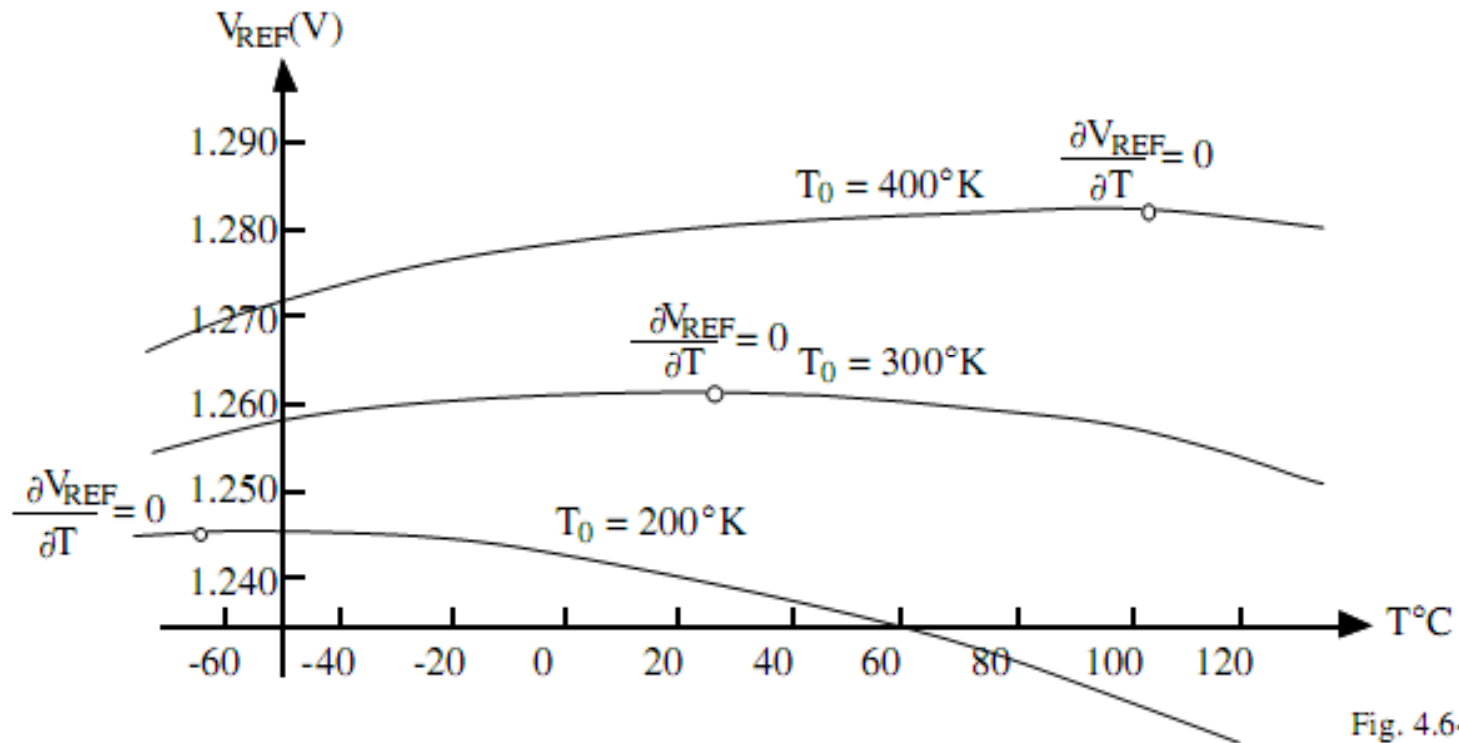

# Bandgap reference

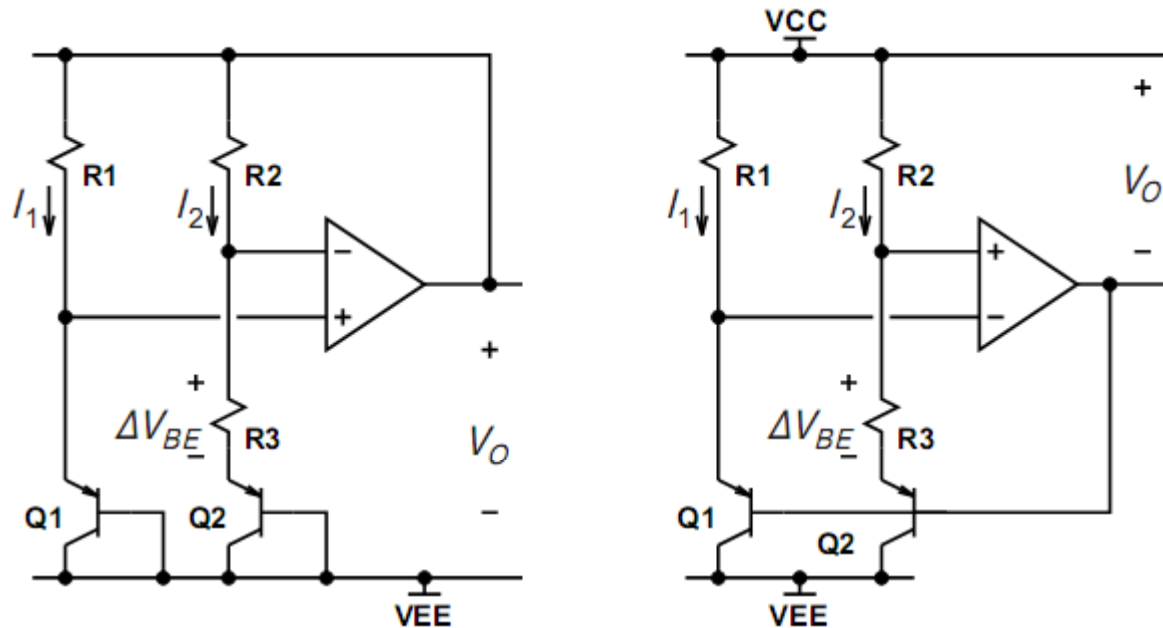

$$\frac{I_1}{I_2} = \frac{R_2}{R_1} \quad V_{R2} = \frac{R_2}{R_3} \Delta V_{BE} \quad \Delta V_{BE} = U_T \ln \left( \frac{I_1}{I_2} \cdot \frac{I_{S2}}{I_{S1}} \right) = U_T \ln \left( \frac{R_2}{R_1} \cdot \frac{I_{S2}}{I_{S1}} \right)$$

$$V_O = |V_{BE1}| + V_{R2} = |V_{BE1}| + \frac{R_2}{R_3} \Delta V_{BE} = |V_{BE1}| + U_T \times \frac{R_2}{R_3} \ln \left( \frac{R_2}{R_1} \cdot \frac{I_{S2}}{I_{S1}} \right)$$



# Bandgap reference

---

Let  $Q2=Q3$ ,  $I_{S2}/I_{S1} = n$ , and  $M3=M4=M5$ , then

$$\Delta V = U_T \ln(n)$$

The output voltage,  $V_O$ , and current,  $I_O$ , are thus

$$V_O = V_{BE3} + U_T \cdot y \ln(n) \quad \text{and} \quad I_O = \frac{V_O}{R_x}$$

- A PTAT current from M8 develops a  $U_T$ -dependent voltage across resistor  $R_y$ . A proper choice of the ratio  $y$  can give a band-gap voltage at  $V_O$ .
- All currents are proportional to  $T$ .
- If desired, a temperature-independent output current can be realized by choosing  $y$  to give an appropriate TC to  $V_O$  to cancel the TC of resistor  $R_2$ .