


# CMOS operational amplifier

Apinunt Thanachayanont


# Ideal opamp

---

Single-Ended Output

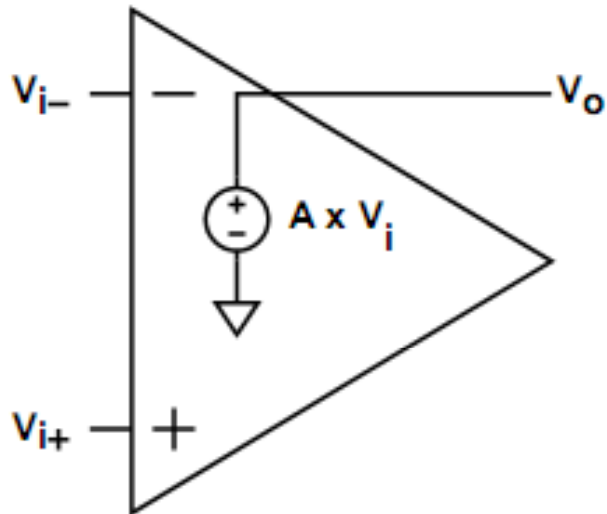


Fully Differential

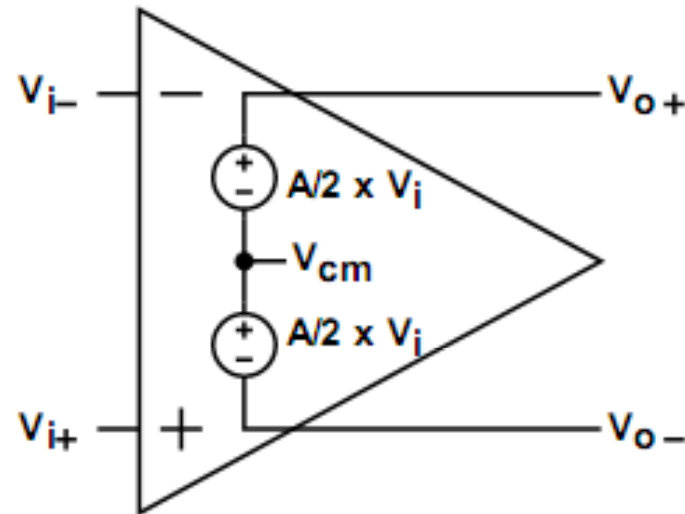


- $V_o = A \times V_i$
- Ideal opamp:
  - $A \rightarrow \infty, Z_{in} \rightarrow \infty, Z_{out} \rightarrow 0.$
  - No frequency dependence.


# Basic 2-stage opamp

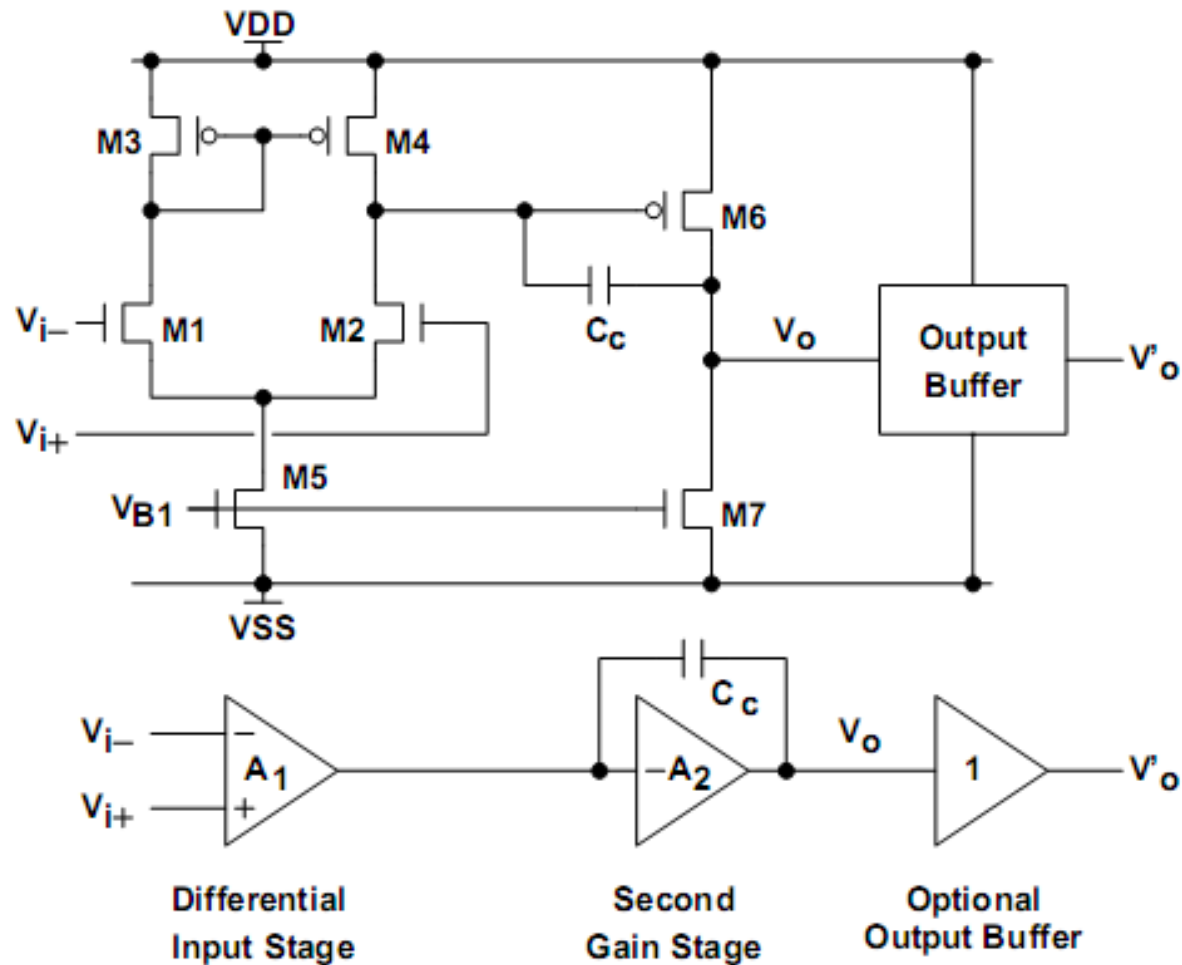

# PMOS input 2-stage opamp

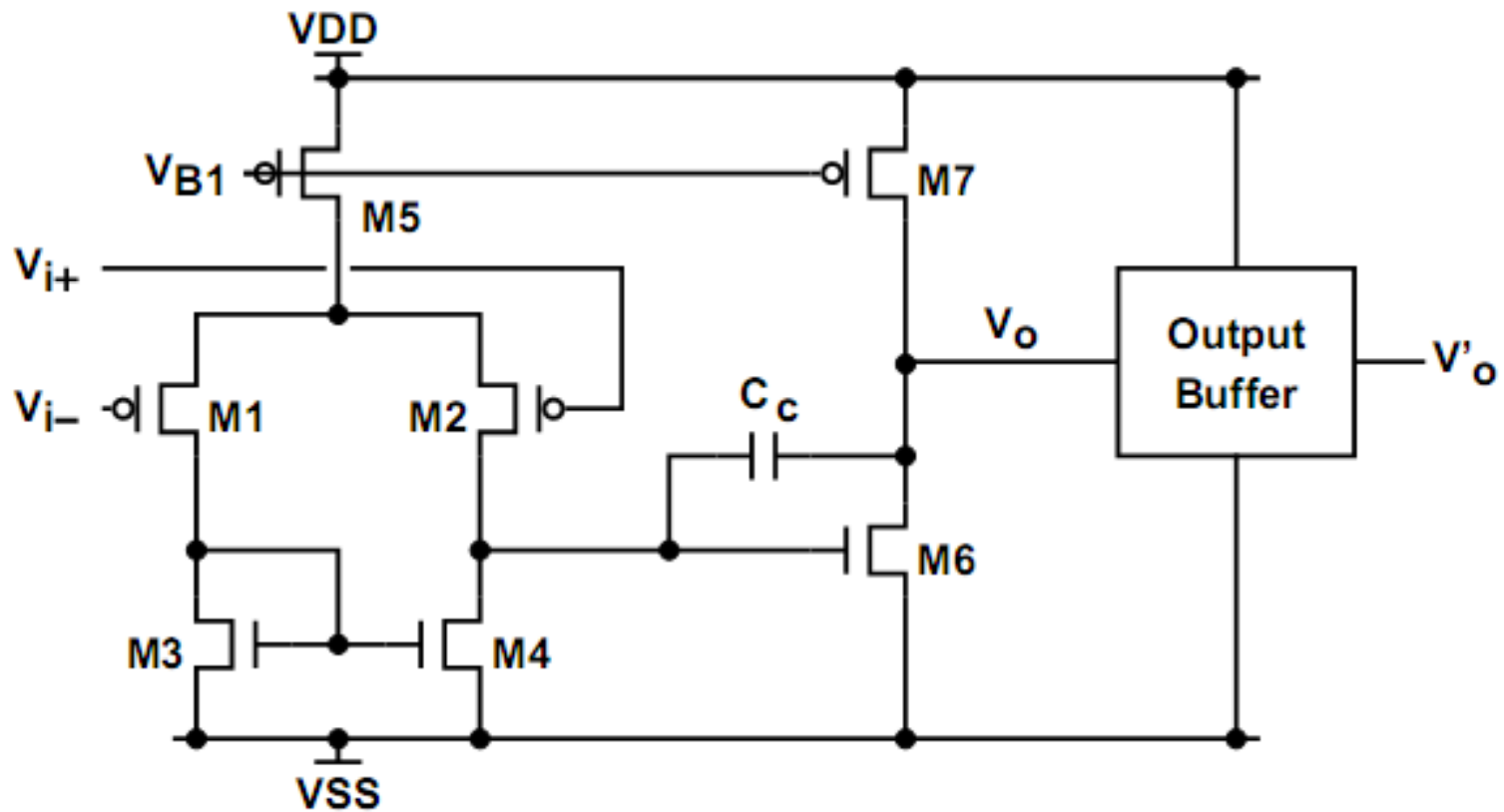

# Constant gm bias generator

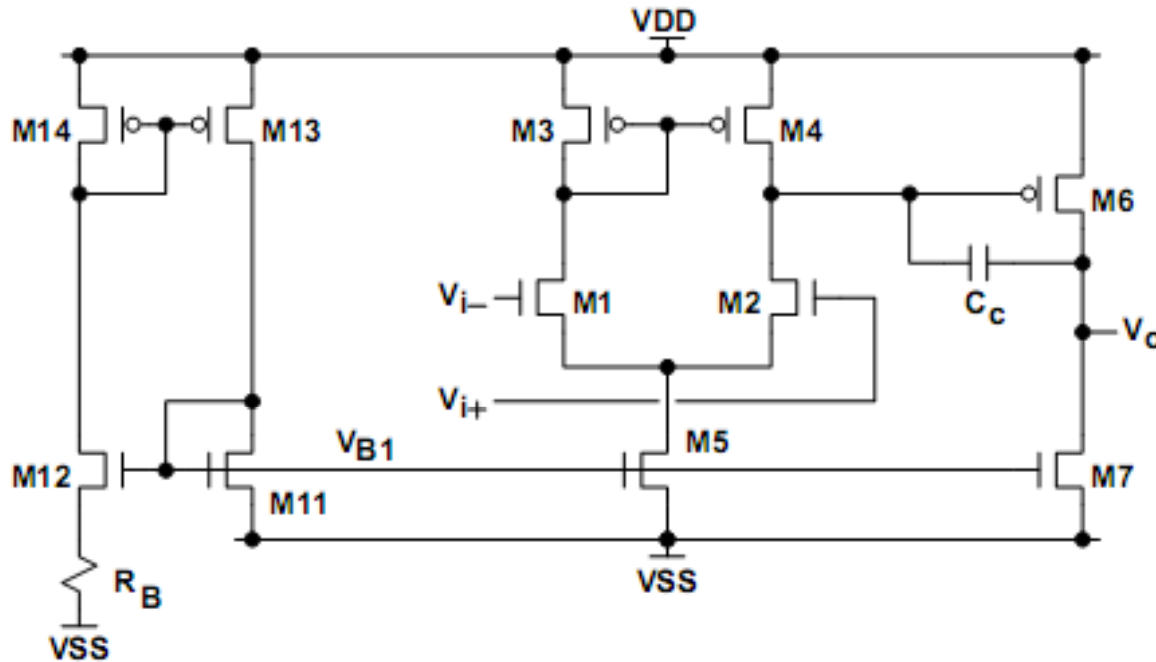

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$


$$\left(\frac{W}{L}\right)_{13} = \left(\frac{W}{L}\right)_{14}$$

$$\left(\frac{W}{L}\right)_{12} = \alpha \cdot \left(\frac{W}{L}\right)_{11}$$

$$g_m = \sqrt{2\mu C_{ox}(W/L)I_D} \quad g_{m11} = \frac{2\sqrt{\alpha}-1}{R_B\sqrt{\alpha}} \quad g_{m1,m2} = g_{m11} \cdot \sqrt{\frac{(W/L)_1}{(W/L)_{11}}} \sqrt{\frac{1}{2} \frac{(W/L)_5}{(W/L)_{11}}}$$

$$g_{m3,m4} = g_{m11} \cdot \sqrt{\frac{\mu_p}{\mu_n}} \sqrt{\frac{(W/L)_3}{(W/L)_{11}}} \sqrt{\frac{1}{2} \frac{(W/L)_5}{(W/L)_{11}}} \quad g_{m6} = g_{m11} \cdot \sqrt{\frac{\mu_p}{\mu_n}} \sqrt{\frac{(W/L)_6}{(W/L)_{11}}} \sqrt{\frac{(W/L)_7}{(W/L)_{11}}}$$

# Simplified 2-stage model

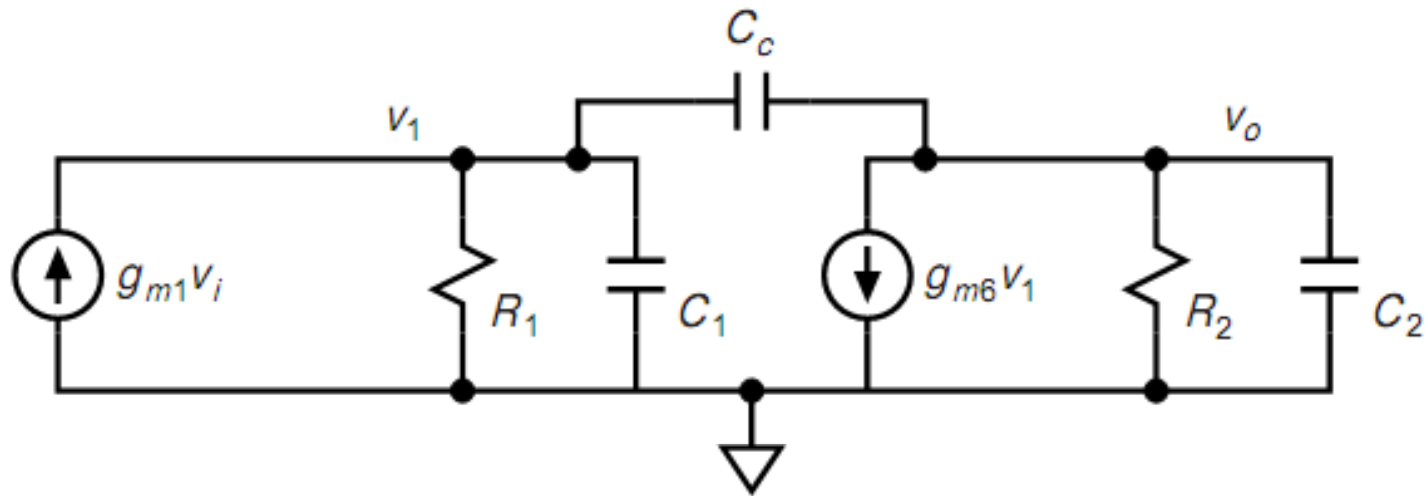

$$G_1 = g_{o2} + g_{o4} \quad G_2 = g_{o6} + g_{o7} \quad C_1 \simeq C_{gs6}$$

$$A_v \equiv \frac{v_o}{v_i} = A_v(0) \frac{1 - s/z_1}{(1 - s/p_1)(1 - s/p_2)}$$

$$A_v(0) = g_{m1}g_{m6}R_1R_2$$

$$p_1 \approx -\frac{g_{m1}}{C_c} \times \frac{1}{A_v(0)} \quad p_2 \approx -\frac{g_{m6}}{C_1 + C_2} \quad z_1 = +\frac{g_{m6}}{C_c}$$



# Frequency compensation using nulling resistor

---

- The zero-nulling resistor  $R_c$  is realized by M10 in the triode region.

$$z_1 = \frac{1}{(1/g_{m6} - R_c)C_c} = -\frac{g_{m6}}{(g_{m6}R_c - 1)C_c}$$

- Let  $\frac{(W/L)_{13}}{(W/L)_{14}} = \frac{(W/L)_{15}}{(W/L)_{16}}$  and  $\frac{(W/L)_7}{(W/L)_{11}} = \frac{(W/L)_6}{(W/L)_{13}}$ , then

$$V_{ov6} = V_{ov13} = V_{ov14} \quad V_{ov10} = V_{ov15} = V_{ov16} \quad \frac{V_{ov6}}{V_{ov10}} = \frac{V_{ov13}}{V_{ov15}} = \sqrt{\frac{(W/L)_{15}}{(W/L)_{13}}}$$

$$g_{m6}R_c = \frac{g_{m6}}{g_{m10}} = \frac{(W/L)_6}{(W/L)_{10}} \frac{V_{ov6}}{V_{ov10}} = \frac{(W/L)_6}{(W/L)_{10}} \sqrt{\frac{(W/L)_{15}}{(W/L)_{13}}}$$

- $p_2/z_1 \approx (g_{m6}R_c - 1)C_c/(C_1 + C_2)$  is independent of process and temperature variations.

# Voltage and current range

---

## Input Common-Mode Range

$$V_{ic(max)} = V_{DD} - V_{GS3} + V_{t1} \quad V_{ic(min)} = V_{SS} + V_{DSAT5} + V_{GS1}$$

- The range is limited to the voltage levels where any transistor goes out of saturation.

## Output Voltage Range

$$V_{o(max)} = V_{DD} - V_{DSAT6} \quad V_{o(min)} = V_{SS} + V_{DSAT7}$$





- Output resistive load can also limit the voltage range, if the available output current is insufficient.

## Maximum Output Current

$$I_{o(sink,max)} = I_{D7} \quad I_{o(source,max)} = \frac{1}{2}k'_p \left(\frac{W}{L}\right)_6 [V_{gs6(max)} - V_{t6}]^2 - I_{D7}$$

$$V_{gs6(max)} = V_{DD} - V_{i+} + V_{t2}$$

# Slew rate

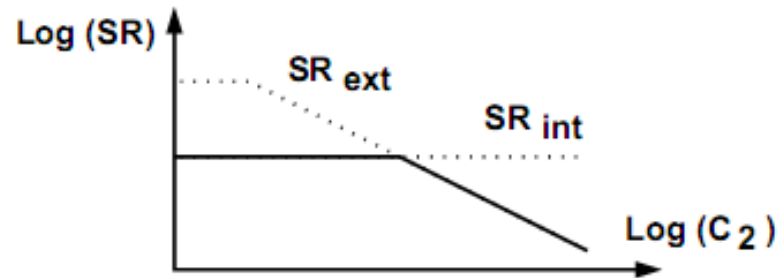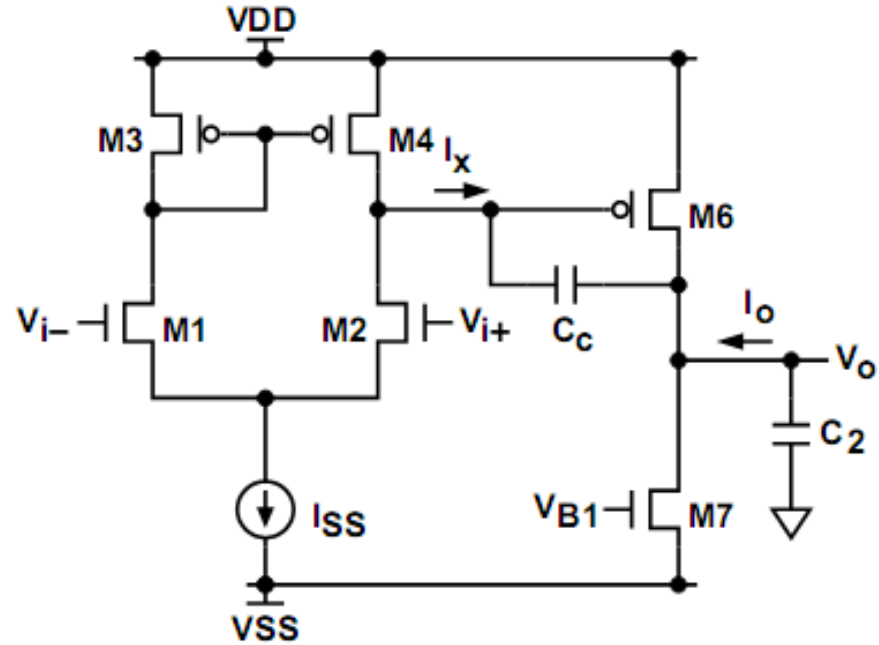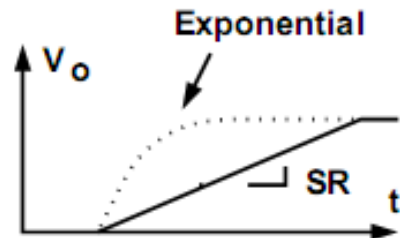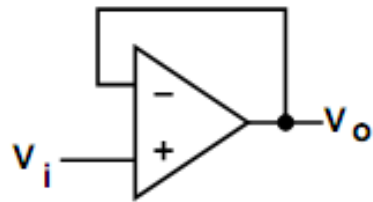

# Slew rate

---

The *internal slew rate* is generally limited by current available to charge and discharge  $C_c$  from input stage. Therefore,

$$\begin{aligned} \text{SR}_{int} &= \left. \frac{dV_o}{dt} \right|_{max} = \frac{I_{x(max)}}{C_c} = \frac{I_{SS}}{C_c} \\ &= \frac{I_{SS}}{g_{m1}} \times \frac{g_{m1}}{C_c} = \frac{I_{SS}}{g_{m1}} \times \omega_u \\ &= (V_{GS1} - V_{t1}) \times \omega_u \\ &= V_{ov1} \times \omega_u \end{aligned}$$

The *external slew rate* is limited by the available current to charge and discharge  $C_2$ . Thus,

$$\text{SR}_{ext} = \frac{I_{D7} - I_{x(max)}}{C_2} = \frac{I_{D7} - I_{SS}}{C_2}$$

# Settling time

---

The frequency response and step response of a single-pole amplifier is

$$A(s) = \frac{A_o}{1 + s/\omega_p} \quad V_o(t) = A_o (1 - e^{-\omega_p t})$$

The settling time can be written as


$$t_s(\epsilon) = \frac{1}{\omega_p} \ln \frac{1}{\epsilon} = \frac{A_o}{\omega_u} \ln \frac{1}{\epsilon}$$

- $\omega_u = A_o \cdot \omega_p$  is the dominant-pole unity-gain frequency.
- $\epsilon = 1 - |V_o(t_s)/A_o|$  is the error when settling occurs.

The 10% to 90% rise time is

$$t_r = \frac{1}{\omega_p} \ln(9) = \frac{2.2}{\omega_p} = \frac{0.35}{f_p} \quad \omega_p = 2\pi f_p$$
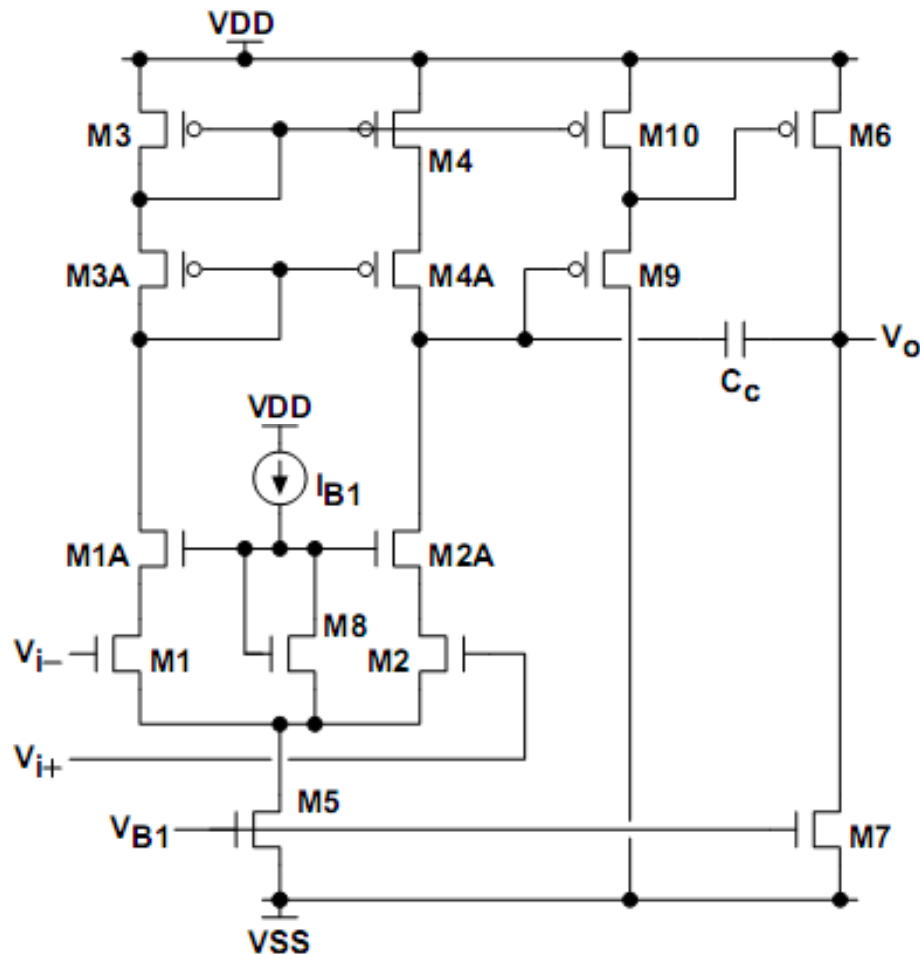
# Two-Stage cascode Operational Amplifier




- The voltage gain  $A_v \propto (g_m r_o)^3$ .
- Size M8 so that

$$V_{DS1} = V_{DS2} \approx V_{DSAT}$$

- Input common-mode range is reduced by cascodes.
- The additional poles are non-dominant and located near  $\omega_T$ .
- The 2nd stage can also use cascodes.



# Current-mirror opamp

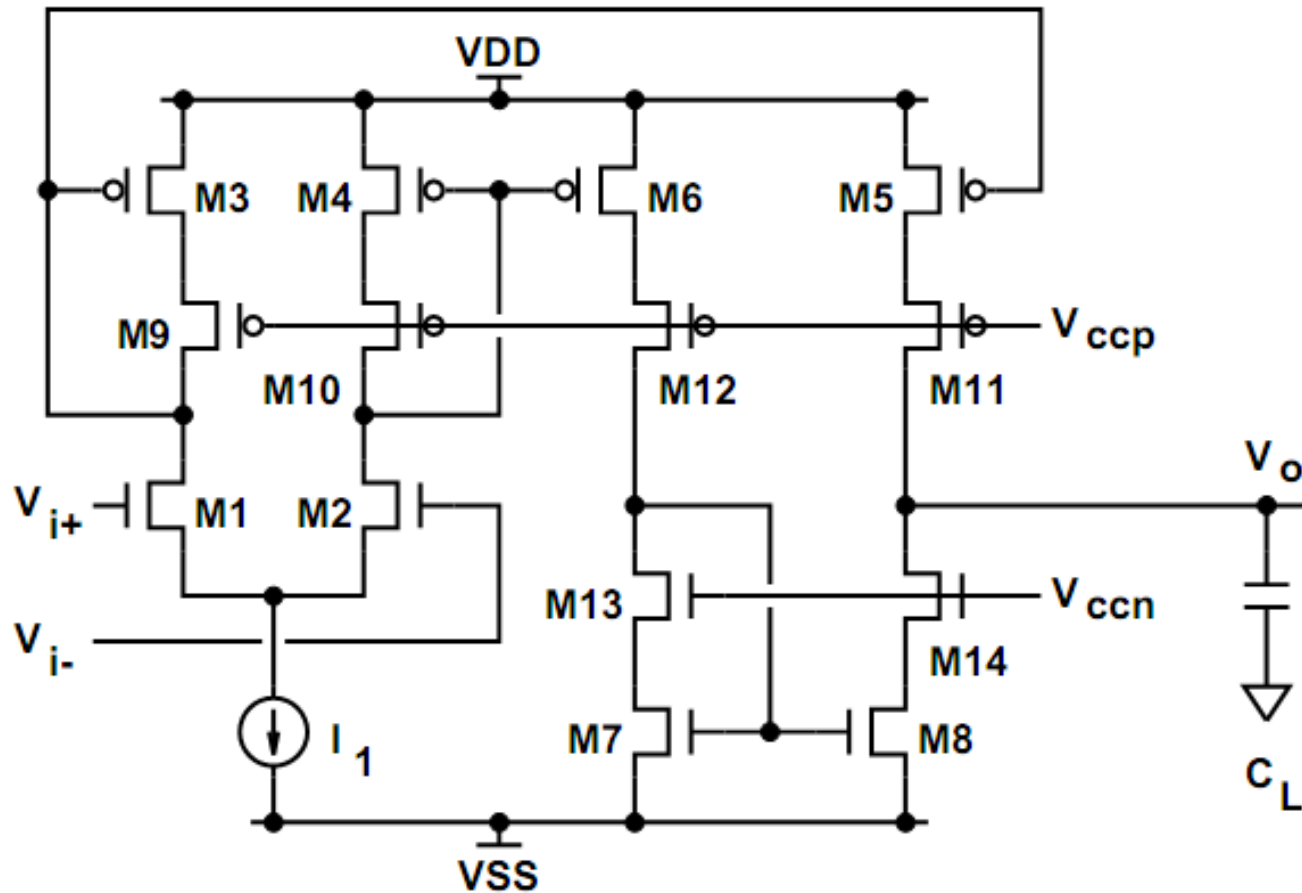

# Current-mirror opamp

---

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_6 = \frac{1}{K} \left(\frac{W}{L}\right)_5 \quad \left(\frac{W}{L}\right)_7 = \frac{1}{K} \left(\frac{W}{L}\right)_8$$

$$I_{D1,D2} = I_{D3,D4} = I_{D6} = I_{D7} = \frac{1}{K} I_{D5} = \frac{1}{K} I_{D8} = \frac{1}{2} I_1 \quad \text{SR} = \frac{K I_1}{C_L}$$

$$A_v(0) = K g_{m1} R_o \quad R_o = \frac{1}{\frac{g_{o5}}{g_{m11} r_{o11}} + \frac{g_{o8}}{g_{m14} r_{o14}}} \quad p_1 = -\frac{1}{R_o C_L} \quad \omega_u = \frac{K g_{m1}}{C_L}$$

- For a given power dissipation, the current-mirror opamps have larger bandwidth and SR than the folded-cascode opamps. But they also suffer from larger thermal noise.
- For small  $C_L$ ,  $K$  may have to be reduced to prevent the nondominant poles from degrading the phase margin.
- A practical upper limit on  $K$  is around 5. For a general-purpose opamp,  $K \simeq 2$ .